

ECE 2101L
Electrical Circuit Analysis II Laboratory

Lab 7
Input and Output Impedances of AC Black Boxes

Report


Choi Tim Antony Yung

April 5, 2020

Objective

The purpose of this experiment is to study the method of determining input and output impedances of AC black boxes from measurements.

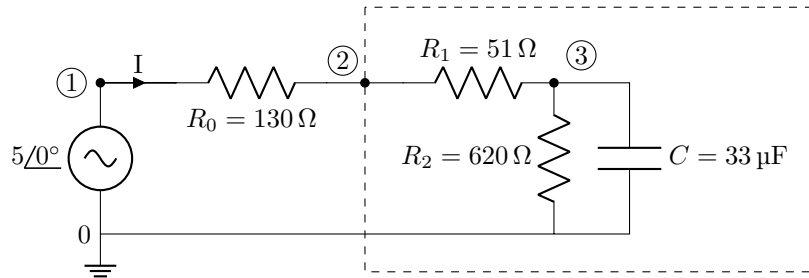1 Measuring input impedance of a black box



The screenshot shows the LTSpice XVII interface. The main window displays the circuit description for a file named "ECE2101L_Lab7_B2.cir". The description includes the following components and their values:

- V1 1 0 AC 5 0: AC voltage source with magnitude of 5V and phase of 0, with node 1 as + terminal and node 0 (ground) at - terminal.
- R0 1 2 130: Resistor 0 from node 1 to node 2 with 130 ohm.
- R1 2 3 51: Resistor 1 from node 2 to node 3 with 51 ohm.
- R2 3 0 620: Resistor 2 from node 3 to node 0 (ground) with 620 ohm.
- C0 3 0 33u: Capacitor 0 from node 3 to node 0 (ground) with 33 microFarad. u denotes micro.

The simulation is performed using the command `.AC LIN 1 60 60`, which performs AC analysis with one frequency value (from 60 Hz to 60 Hz). The results are printed using `.PRINT AC v(2)` (Print the voltage at node 2, relative to ground) and `.PRINT AC i(R0)` (Print the current flowing through R0).

The simulation results are displayed in a window titled "ECE2101L Lab7 Part B2: Measuring INPUT impedance of a black box". The results are as follows:

--- AC Analysis ---			
frequency:	60	Hz	
V(2):	mag: 2.41621	phase: -29.7742°	voltage
I(R0):	mag: 0.0241612	phase: 22.4577°	device_current

Figure 1: Screenshot of circuit description used and the simulation result

Procedure

A SPICE netlist was written to simulate the above circuit with LTspice XVI, the netlist is attached at the back of this report. The current of R_0 was used to determine I .

Result


V_2 calculated	I calculated	Z_{in} calculated
2.41621 $\angle -29.7742^\circ$ V	0.0241612 $\angle 22.4577^\circ$ A	100.0037 $\angle -52.2319^\circ \Omega$

V_2 measured	I measured	Z_{in} measured	$ Z_{in} $	Error
2.41621 $\angle -29.7742^\circ$ V	0.0241612 $\angle 22.4577^\circ$ A	100.0037 $\angle -52.2319^\circ \Omega$		0 %

Analysis

As the above measurement was simulated, there is no error. However, were it to be measured from an actual circuit, the measurement would be subjected to errors due to variation of impedance from its nominal value, imprecise oscilloscope measurement, dissipation of energy from nonideal wire, and noise from electromagnetic interferences, to name a few. Possible improvements to the above problem includes measuring impedances with LCR meter and adjusting impedance by adding small impedances, avoiding long wires, and spacing apart components, et cetera.

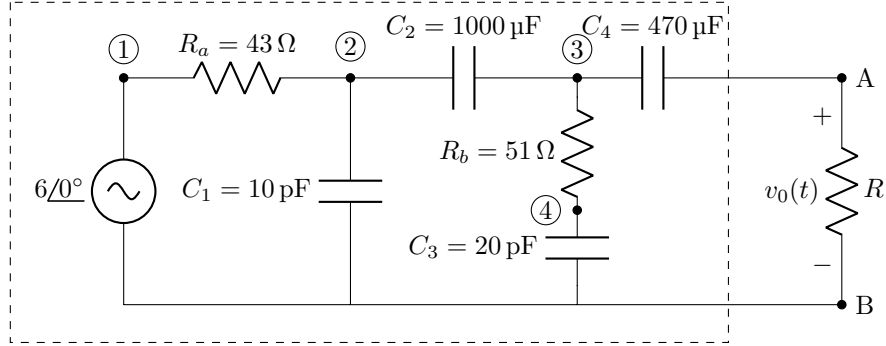2 Measuring output impedance of a black box



Theory

With V_{th} as the open circuit voltage difference of A and B, and V_{01} and V_{02} as the voltage of $R = 130\Omega$ and $R = 130\Omega$ respectively, the magnitude of output impedance R_{out} and X_{out} can be found by solving the following system of equations:

$$|V_{01}| = \frac{R_1}{\sqrt{(R_1 + R_{out})^2 + (X_{out})^2}} |V_{th}|$$

$$|V_{02}| = \frac{R_2}{\sqrt{(R_2 + R_{out})^2 + (X_{out})^2}} |V_{th}|$$

... which can be simplified to the following:

$$(R_1 + R_{out})^2 + (X_{out})^2 = \left(\frac{R_1}{|V_{01}|} |V_{th}| \right)^2$$

$$(R_2 + R_{out})^2 + (X_{out})^2 = \left(\frac{R_2}{|V_{02}|} |V_{th}| \right)^2$$

By solving the above system of equation above, we can determine the magnitude of R_{out} and X_{out} .

Procedure

A SPICE netlist was written for the blackbox subcircuit, and three separate netlists was written to simulate, in LTspice XVI, the above circuit with A to B open or with different value of resistance attached to A and B, the netlists are attached at the back of this report.

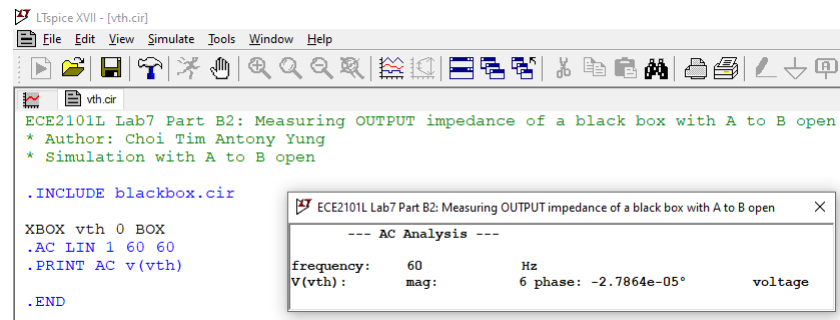


Figure 2: Screenshot of circuit description used and the simulation result leaving A and B open

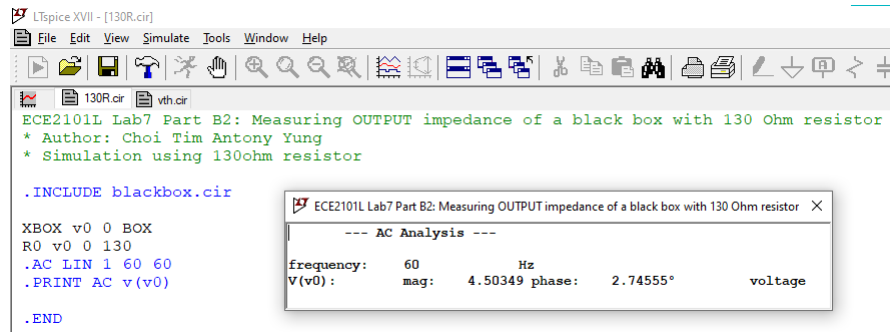


Figure 3: Screenshot of circuit description used and the simulation result with $130\ \Omega$ resistor attached

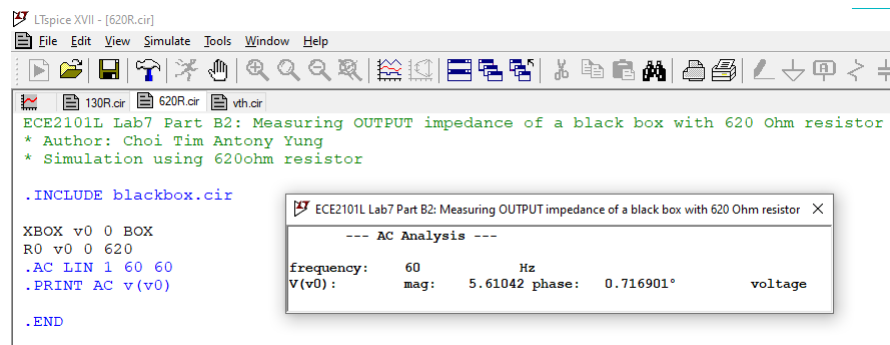


Figure 4: Screenshot of circuit description used and the simulation result with $620\ \Omega$ resistor attached

Result

R	$ V_{th} $ measured	$ V_0 $ measured	$ R_{out} $ calculated	$ X_{out} $ calculated
130 Ω	6 V	4.503 49 V	43 Ω	8.3 Ω
620 Ω	6 V	5.610 42 V		

Analysis

After obtaining the value of the output impedance, we can repeat the measurement with an inductor L attached in series before R. In theory, if X_{out} is inductive and therefore positive, then adding L in series will increase the magnitude of total reactance. Whereas if X_{out} is capacitive therefore negative, then adding L, a positive reactance, in series will decrease the magnitude of total reactance. Therefore, if the measurement of $|X_{out}|$ after adding L is larger than before, then X_{out} is inductive and therefore positive, otherwise, it is capacitive and therefore negative.

```
1 ECE2101L Lab7 Part B2: Measuring INPUT impedance of a black box
2 * Author: Choi Tim Antony Yung
3
4 V1 1 0 AC 5 0
5 * AC voltage source with magnitude of 5V and phase of 0
6 * with node 1 as + terminal and node 0 (ground) at - terminal
7
8 R0 1 2 130
9 * Resistor 0 from node 1 to node 2 with 130 ohm
10
11 R1 2 3 51
12 * Resistor 1 from node 2 to node 3 with 51 ohm
13
14 R2 3 0 620
15 * Resistor 2 from node 3 to node 0 (ground) with 620 ohm
16
17 C0 3 0 33u
18 * Capacitor 0 from node 3 to node 0 (ground) with 33 microFarad
19 * u denotes micro
20
21 .AC LIN 1 60 60
22 * perform AC analysis with one frequency value (from 60 Hz to 60 Hz)
23
24 .PRINT AC v(2)
25 * Print the voltage at node 2, relative to ground
26
27 .PRINT AC i(R0)
28 * Print the current flowing through R0
29
30 .END
31
```

```
1 * ECE2101L Lab7 Part B2: Measuring OUTPUT impedance of a black box
2 * Author: Choi Tim Antony Yung
3 * Definition of blackbox subcircuit
4
5 .SUBCKT BOX A B
6 V1 1 B AC 6 0
7 Ra 1 2 43
8 C1 2 B 10p
9 C2 2 3 1000u
10 Rb 3 4 51
11 C3 4 B 20p
12 C4 3 A 470u
13 .ENDS
```



```
1 ECE2101L Lab7 Part B2: Measuring OUTPUT impedance of a black box with A to B open
2 * Author: Choi Tim Antony Yung
3 * Simulation with A to B open
4
5 .INCLUDE blackbox.cir
6
7 XBOX vth 0 BOX
8 .AC LIN 1 60 60
9 .PRINT AC v(vth)
10
11 .END
```

```
1 ECE2101L Lab7 Part B2: Measuring OUTPUT impedance of a black box with 130 Ohm
  resistor
2 * Author: Choi Tim Antony Yung
3 * Simulation using 130ohm resistor
4
5 .INCLUDE blackbox.cir
6
7 XBOX v0 0 BOX
8 R0 v0 0 130
9 .AC LIN 1 60 60
10 .PRINT AC v(v0)
11
12 .END
13
```

```
1 ECE2101L Lab7 Part B2: Measuring OUTPUT impedance of a black box with 620 Ohm
  resistor
2 * Author: Choi Tim Antony Yung
3 * Simulation using 620ohm resistor
4
5 .INCLUDE blackbox.cir
6
7 XBOX v0 0 BOX
8 R0 v0 0 620
9 .AC LIN 1 60 60
10 .PRINT AC v(v0)
11
12 .END
```