

ECE2101L  
Electrical Circuit Analysis II Laboratory


Lab 9  
Real, Reactive, Complex Power and Power Factor

Report

Choi Tim Antony Yung

April 12, 2020
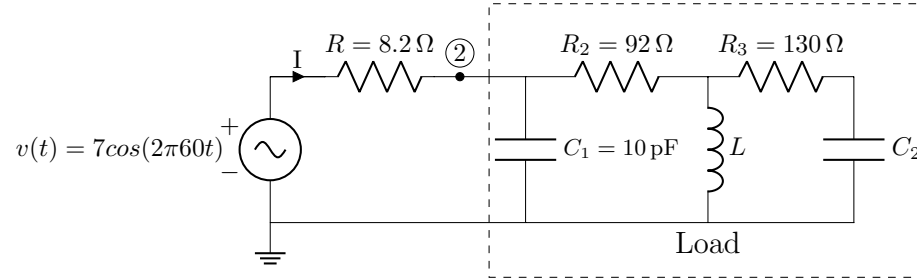
# 1 Determination of load power using oscilloscope



## Procedure

The above circuit was simulated with LTspice XVI with the RMS value of source voltage.

## Result

Variant	$V_2$ RMS calculated	$I$ RMS calculated	P calculated	Q calculated
original	4.59698/ <u>1.66598°</u> V	46.2263/ <u>-20.6450°</u> mA	0.196593 W	0.0806727 VAR

Variant	$V_2$ RMS measured	$I$ RMS measured	P measured	Q measured	P error	Q error
original	4.59698/ <u>1.66595°</u> V	46.2259/ <u>-20.6449°</u> mA	0.196591 W	0.0806715 VAR	0.00%	0.00%
$C_2 = 1000 \mu\text{F}$	4.61679/ <u>1.31314°</u> V	42.7464/ <u>-17.5681°</u> mA	0.186732 W	0.0638643 VAR	N/A	
$L = 0.4 \text{ H}$	4.83025/ <u>2.21037°</u> V	27.2304/ <u>-56.5461°</u> mA	0.068221 W	0.1124540 VAR		

Variant	Load total Z calculated	$ S $ calculated	PF measured
original	99.4451/ <u>22.3110°</u> Ω	0.212501 VA	0.925138 lagging
$C_2 = 1000 \mu\text{F}$	No calculation		0.946191 lagging
$L = 0.4 \text{ H}$			0.518677 lagging

## Analysis

From the result we observed that the load power factor have no relation to the magnitude of the load current. The power factor increase with increase of capacitance and decrease with increase of inductance. The angle of load total impedance is the same as the load power angle. Power factor increases with decrease of load power angle and vice versa.

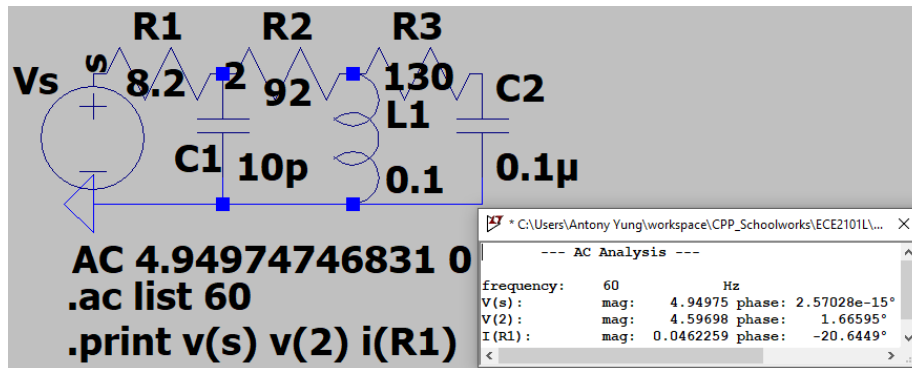


Figure 1: Simulation of the original circuit

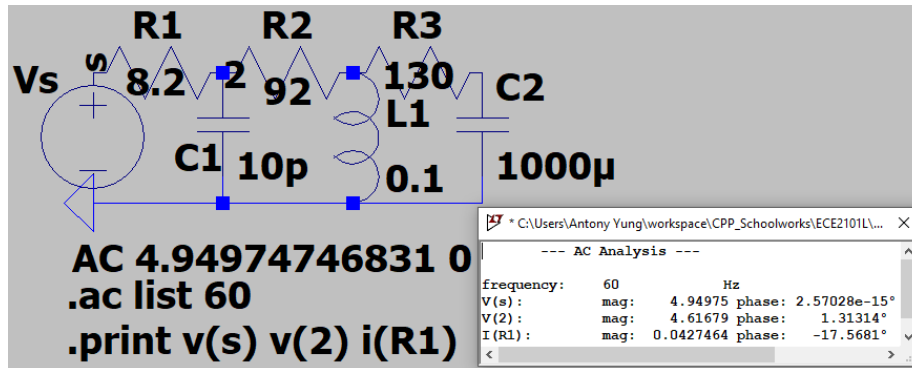


Figure 2: Simulation of the  $C_2 = 1000 \mu\text{F}$  circuit

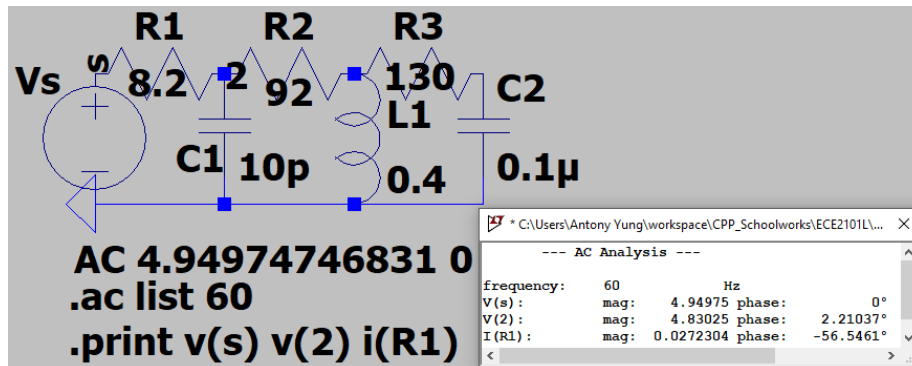


Figure 3: Simulation of the  $L = 0.4 \text{ H}$  circuit

## 2 Determination of load real power using multimeter

### Procedure

The original circuit was simulated with LTspice XVI with the RMS value of source voltage and current of  $R_2$  and  $R_3$ .

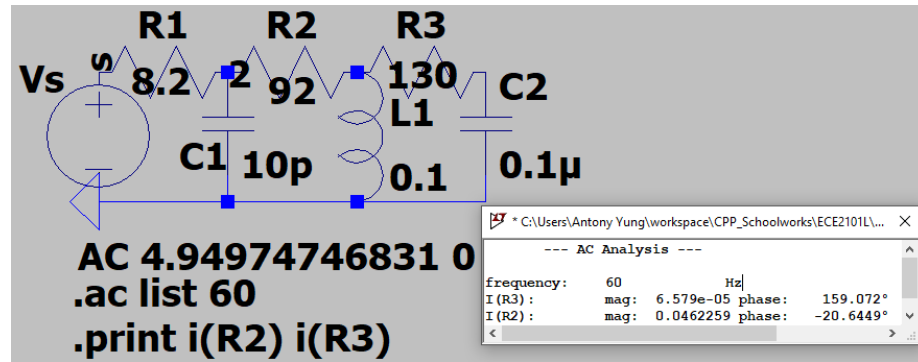


Figure 4: Simulation of the original circuit with measurement of  $I_2$  and  $I_3$

### Result

Variant	P from B1 measured	$I_2$ RMS measured	$I_3$ RMS measured	P measured	P error
original	0.196591 W	46.2259/ <u>-20.6449°</u> mA	65.79/ <u>159.072°</u> $\mu$ A	0.196589 W	0.00%