

ECE 2200L
Introduction to Microelectronics Circuits
Laboratory

Experiment 4
Zener Diode I-V Characteristics

Report

Choi Tim Antony Yung

October 7, 2020

Objective

To study the current-voltage relationship of a Zener diode, to determine the reverse saturation current, the ideality factor (η) in the forward region, the Zener voltage and the Zener resistance (R_Z) in the Zener region.

Result

The following is the experimental data obtained from 1N4733 Zener diode.

	V_d (V)	I_d (A)	$\frac{V_d}{V_T}$	$\ln(I_d)$ (A)
Reverse Breakdown	-5.175	-3.051×10^{-2}		
	-5.137	-1.808×10^{-2}		
	-5.112	-1.034×10^{-2}		
	-5.089	-4.790×10^{-3}		
Reverse Bias	-4.749	-2.200×10^{-4}		
	-4.553	-1.031×10^{-4}		
	-3.568	-5.500×10^{-6}		
	-2.088	-2.000×10^{-7}		
	-1.055	-1.000×10^{-7}		
	0.337	$0.000 \times 10^{+0}$		
Forward Bias	0.654	1.570×10^{-4}	25.15385	-8.75926
	0.753	4.355×10^{-3}	28.96154	-5.43643
	0.772	8.420×10^{-3}	29.69231	-4.77715
	0.783	1.218×10^{-2}	30.11538	-4.40796
	0.793	1.657×10^{-2}	30.50000	-4.10016
	0.799	2.067×10^{-2}	30.73077	-3.87907
	0.805	2.494×10^{-2}	30.96154	-3.69128

From the $\frac{V_d}{V_T}$ vs $\ln(I_d)$ chart (2), the ideality of the diode η can be derived from reciprocal of the slope of line of best fit:

$$\eta = \frac{1}{0.8739} = 1.144$$

From the reverse bias portion of data we can assert that the reverse saturation current of the Zener diode is around 0.1 μ A to 0.2 μ A.

From the IV chart at reverse breakdown region (3) we can derive the Zener resistance from reciprocal of the slope of line of best fit:

$$R_Z = \frac{1}{0.3021} = 3.31 \Omega$$

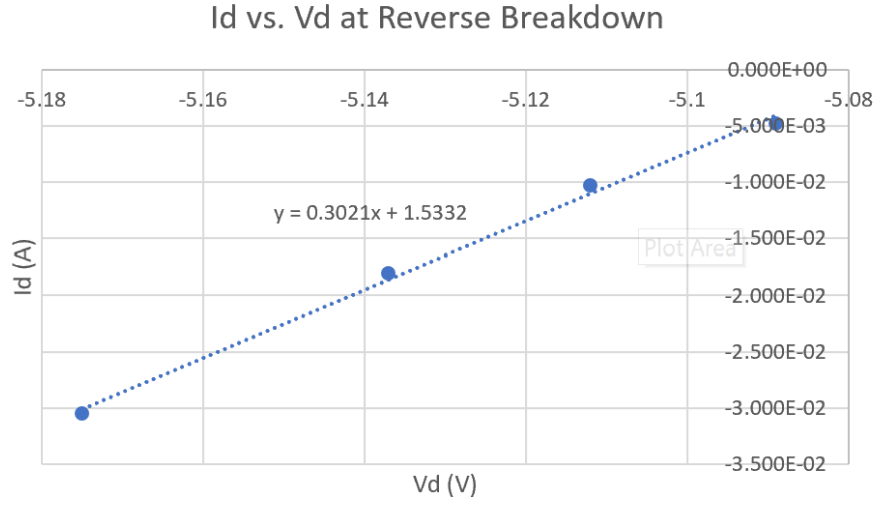


Figure 3: IV chart of 1N4733 Zener Diode at reverse breakdown region

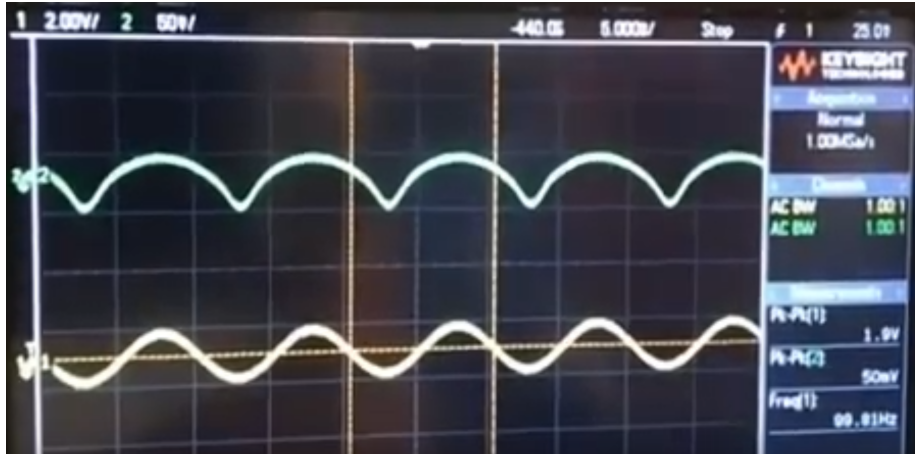


Figure 4: Oscilloscope displaying source and output voltage of part 3 circuit

The AC component of the source voltage and output voltage measured in part 3 are $V_S = 1.9\text{ V}$ and $V_O = 50\text{ mV}$. The Regulator Rejection Ratio is then:

$$RRR = 20 \log_{10} \left(\frac{V_O}{V_S} \right) = 20 \log_{10} \left(\frac{0.050}{1.9} \right) = -31.6 \text{ dB}$$

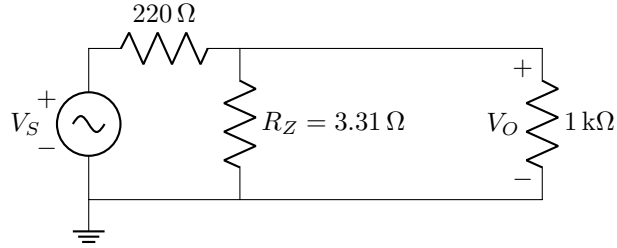


Figure 5: Small signal model of part 3 circuit

The RRR can also be derived from the small signal analysis using Zener resistance:

$$RRR = 20 \log_{10} \left(\frac{V_O}{V_S} \right) = 20 \log_{10} \left(\frac{R_Z || 1000}{220 + (R_Z || 1000)} \right) = 20 \log_{10} \left(\frac{3.3}{223.3} \right) = -35.8 \text{ dB}$$

Conclusion

As can be seen above, the ideality factor and Zener resistance can be derived from the IV characteristic chart of the Zener diode. Also, the RRR derived from measured value is higher than the RRR derived from small signal model of the circuit. This could be a result of noise increasing the magnitude of output voltage that in turn increased the output to source voltage ratio.