

ECE 2300L  
Digital Logic Design Laboratory


Experiment 11

Report

Choi Tim Antony Yung

April 23, 2020

## State Diagram

 


## State Table

$A$	$B$	$A^+$	$B^+$	$T_A$	$T_B$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1


## Truth Table

$A$	$B$	$T_A$	$A$	$B$	$T_B$
0	0	0	0	0	1
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	1

## Karnaugh Maps

 


$$T_A = B$$

 

$$T_B = 1$$

## Schematic

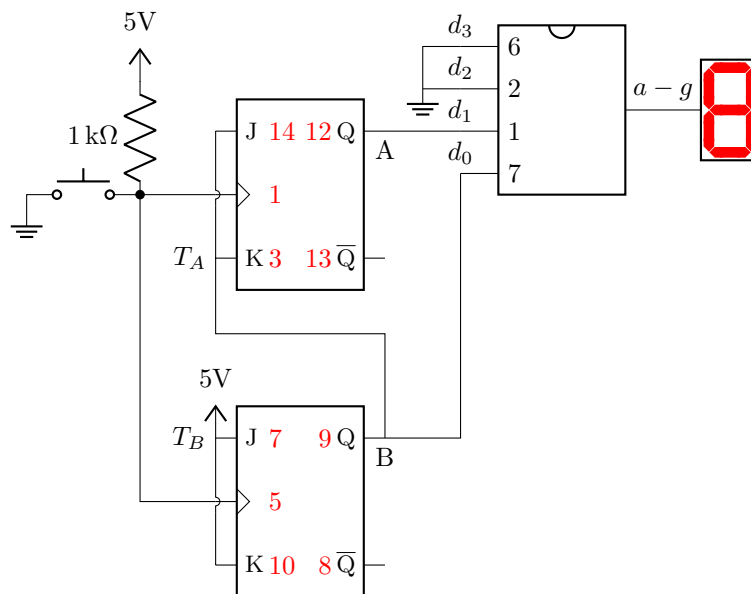




# DUAL JK NEGATIVE EDGE-TRIGGERED FLIP-FLOP

The SN54LS/74LS73A offers individual J, K, clear, and clock inputs. These dual flip-flops are designed so that when the clock goes HIGH, the inputs are enabled and data will be accepted. The logic level of the J and K inputs may be allowed to change when the clock pulse is HIGH and the bistable will perform according to the truth table as long as minimum set-up times are observed. Input data is transferred to the outputs on the negative-going edge of the clock pulse.

LOGIC DIAGRAM (Each Flip-Flop)

 

MODE SELECT — TRUTH TABLE

OPERATING MODE	INPUTS			OUTPUTS	
	$\overline{C_D}$	J	K	Q	$\overline{Q}$
Reset (Clear)	L	X	X	L	H
Toggle	H	h	h	$\overline{q}$	q
Load "0" (Reset)	H	l	h	L	H
Load "1" (Set)	H	h	l	H	L
Hold	H	l	l	q	$\overline{q}$

H, h = HIGH Voltage Level


L, l = LOW Voltage Level

X = Don't Care


l, h (q) = Lower case letters indicate the state of the referenced input (or output) one set-up time prior to the HIGH to LOW clock transition.

## SN54/74LS73A

 
### DUAL JK NEGATIVE EDGE-TRIGGERED FLIP-FLOP LOW POWER SCHOTTKY



J SUFFIX  
CERAMIC  
CASE 632-08

 

N SUFFIX  
PLASTIC  
CASE 646-06

 


D SUFFIX  
SOIC  
CASE 751A-02

#### ORDERING INFORMATION

SN54LSXXJ	Ceramic
SN74LSXXN	Plastic
SN74LSXXD	SOIC

#### LOGIC SYMBOL

 

VCC = PIN 4  
GND = PIN 11

## Demo

A video demonstration can be found [here](https://photos.app.goo.gl/729cwgJ9mkX1yE7Z6) at <https://photos.app.goo.gl/729cwgJ9mkX1yE7Z6>

