

ECE 2101L
Electrical Circuit Analysis II Laboratory

Lab 11
Transfer Function of AC Circuits

Prelab

Choi Tim Antony Yung


April 20, 2020

1 Theory of transfer function

According to *Fundamentals of Electric Circuits (2017)*, The transfer function $H(\omega)$ of a circuit is the frequency-dependent ratio of a phasor output $Y(\omega)$ (an element voltage or current) to a phasor input $X(\omega)$ (source voltage or current). [1] As $Y(\omega)$ may have a non-zero phase shift relative to $X(\omega)$, $H(\omega)$ is either real if they have the same phase, or complex otherwise. Given a transfer function $H(\omega)$ and an input voltage $V_{in}(\omega)$, the output voltage $V_{out}(\omega)$ can be calculated:

$$V_{out}(\omega) = H(\omega) \cdot V_{in}(\omega)$$

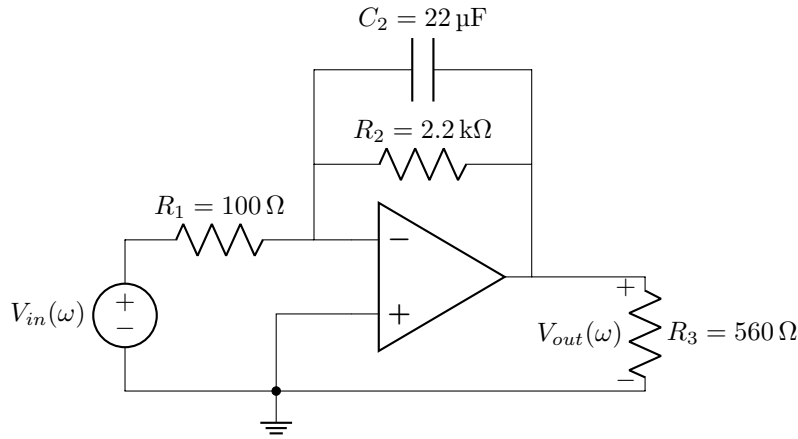2 Transfer function of AC circuit with op amp



Assuming the op amp is ideal, the transfer function $H(\omega)$ can be determined as follow:

$$H(\omega) = \frac{V_{out}}{V_{in}} = -\frac{Z_2}{Z_1} = -\frac{R_2 \parallel Z_{C_2}}{R_1} = -\frac{\frac{1}{\frac{1}{R_2} + j\omega C_2}}{R_1} = -\frac{1}{\frac{R_1}{R_2} + R_1 \omega C_2 j} = \frac{-\frac{R_1}{R_2} + R_1 \omega C_2 j}{(\frac{R_1}{R_2})^2 + (R_1 \omega C_2)^2}$$

$V_{out}(\omega)$ can then be determined as follow:

$$V_{out}(\omega) = \frac{-\frac{R_1}{R_2} + R_1 \omega C_2 j}{(\frac{R_1}{R_2})^2 + (R_1 \omega C_2)^2} V_{in}(\omega)$$

The magnitude of $H(\omega)$ can be determined as follow:

$$|H(\omega)| = \sqrt{\left(\frac{-\frac{R_1}{R_2}}{(\frac{R_1}{R_2})^2 + (R_1 \omega C_2)^2} \right)^2 + \left(\frac{R_1 \omega C_2}{(\frac{R_1}{R_2})^2 + (R_1 \omega C_2)^2} \right)^2} = \frac{1}{\sqrt{(\frac{R_1}{R_2})^2 + (R_1 \omega C_2)^2}}$$

The phase of $H(\omega)$ can be determined as follow:

$$\arg(H(\omega)) = \tan^{-1} \left(\frac{\frac{R_1 \omega C_2}{(\frac{R_1}{R_2})^2 + (R_1 \omega C_2)^2}}{-\frac{R_1}{R_2}} \right) = \tan^{-1} \left(\frac{R_1 \omega C_2}{-\frac{R_1}{R_2}} \right) = \tan^{-1} (-R_2 \omega C_2)$$

When $R_1 = 100 \Omega$, $R_2 = 2.2 \text{ k}\Omega$, $R_3 = 560 \Omega$, $C_2 = 22 \mu\text{F}$, $\omega = 2\pi 60 \text{ rad/s}$:

$$H(\omega) = \frac{1}{\sqrt{(\frac{R_1}{R_2})^2 + (R_1 \omega C_2)^2}} \angle \tan^{-1} (-R_2 \omega C_2)$$

$$H(2\pi 60) = \frac{1}{\sqrt{(\frac{100}{2200})^2 + ((100)(2\pi 60)(22) \times 10^{-6})^2}} \angle \tan^{-1} (-(2200)(2\pi 60)(22) \times 10^{-6})$$

$$H(2\pi 60) = 1.203913 \angle -86.8630^\circ$$

References

- [1] C.K. Alexander and M.N.O. Sadiku. *Fundamentals of Electric Circuits*. COLLEGE IE OVERRUNS. McGraw-hill Education, 2017. ISBN: 9781259251320. URL: <https://books.google.com/books?id=e4-gjwEACAAJ>.