

ECE 2300L  
Digital Logic Design Laboratory


Experiment 12

Report


Choi Tim Antony Yung

May 12, 2020


## Pulse Generator Using 555 Timer

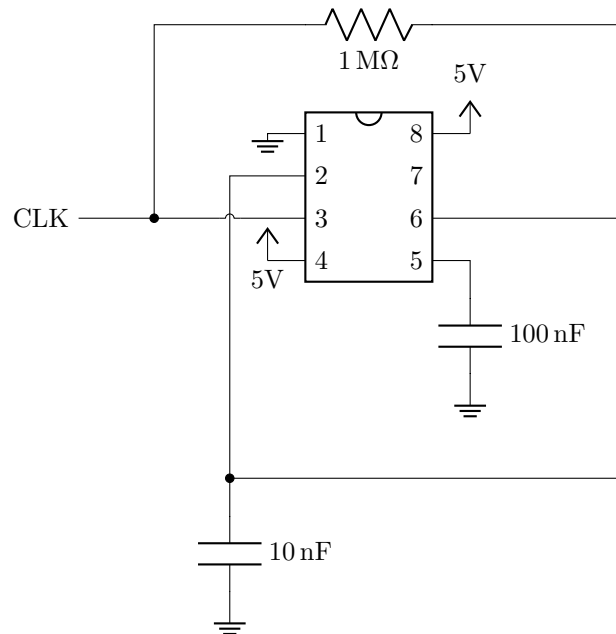

## Pulse Generator Using Inverter

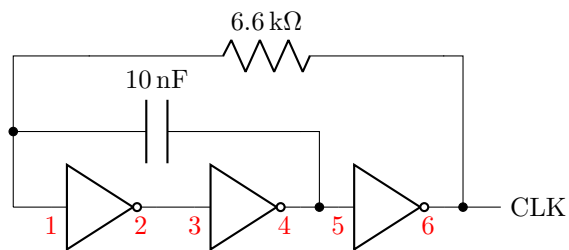

## State Diagram

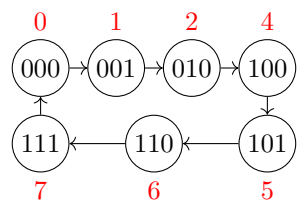

## State Table

$A$	$B$	$C$	$A^+$	$B^+$	$C^+$	$T_A$	$T_B$	$T_C$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	1	0	0	1	1	0
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

## Truth Table

$A$	$B$	$C$	$T_A$	$A$	$B$	$C$	$T_B$	$A$	$B$	$C$	$T_C$
0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	0	1	0	1	0	1	0	0
1	0	0	0	1	0	0	0	1	0	0	1
1	0	1	0	1	0	1	1	1	0	1	1
1	1	0	0	1	1	0	0	1	1	0	1
1	1	1	1	1	1	1	1	1	1	1	1

## Karnaugh Maps

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0			X	1
	1			1	

$$T_A = BC + \overline{A}B$$


		<i>BC</i>			
		00	01	11	10
<i>A</i>	0		1	X	1
	1		1	1	

$$T_B = C + \overline{A}B$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	1	1	X	
	1	1	1	1	1

$$T_C = A + \overline{B}$$



## Schematic

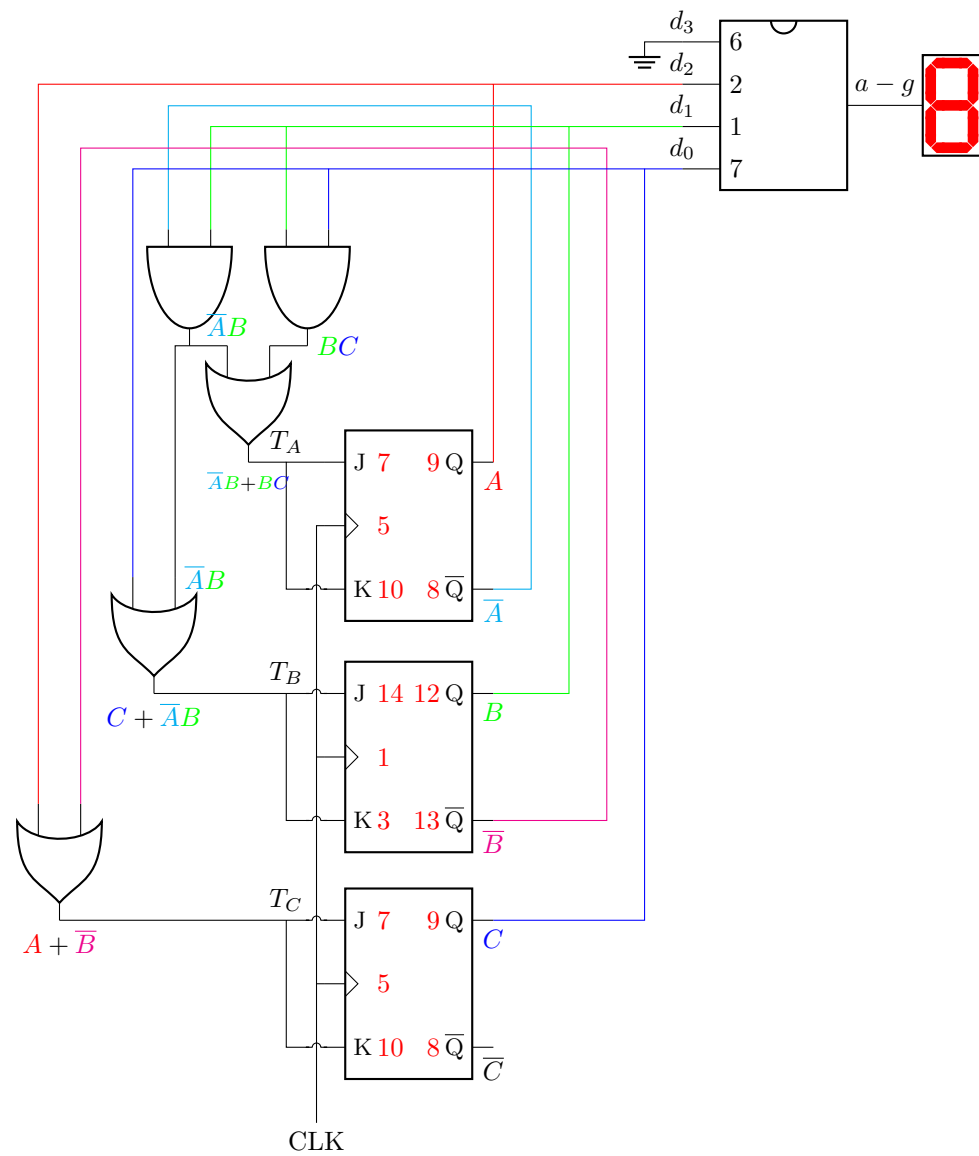

## Demo

Video demonstrations can be found [here](https://photos.app.goo.gl/eSdNj98HEJmizMVE7) at <https://photos.app.goo.gl/eSdNj98HEJmizMVE7>

### Pulse Generator

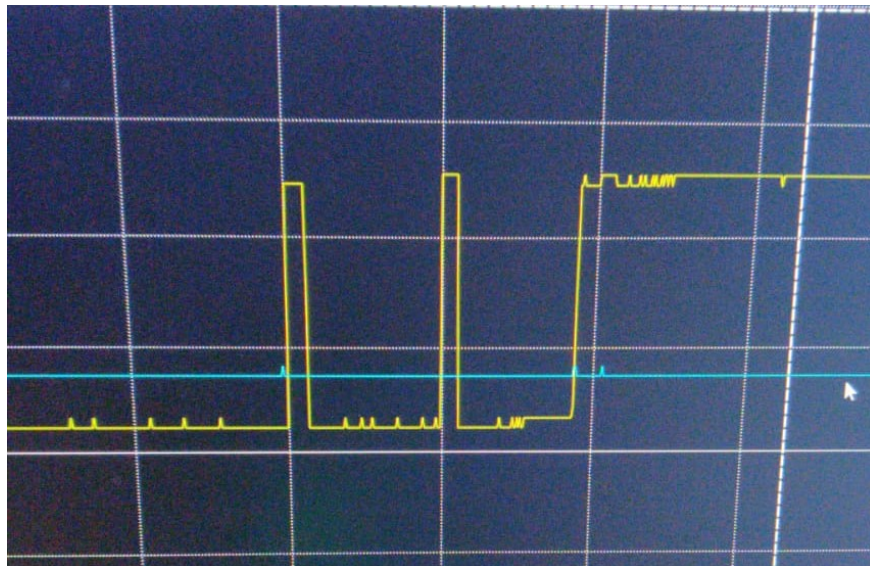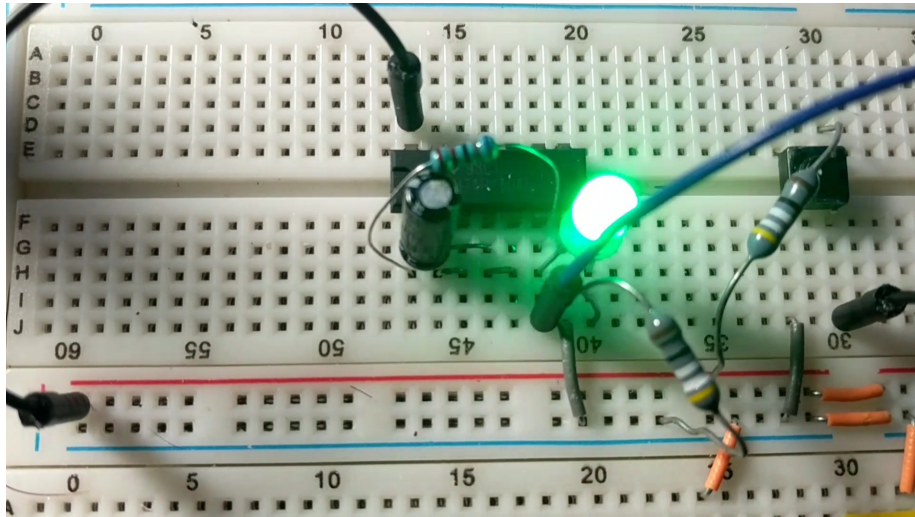

As seen from the oscilloscope capture above, the pulse generator have multiple rising edges at the start of the pulse, therefore it is not suitable to be used as clock. For the counter, a push button was used instead.

## Counter

