

ECE 2200L  
Introduction to Microelectronics Circuits  
Laboratory

Experiment 6  
Bipolar Junction Transistor Biasing Circuits and  
Bias Point Stability

Report

Choi Tim Antony Yung

October 21, 2020

## Objective

To study and experiment on three types of DC biasing circuits for BJTs, and compare the stability of the bias point in these circuits.

## Prelab

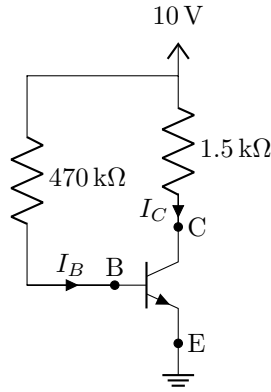


Figure 1: Circuit 1

Assuming  $V_{BE} = 0.7\text{ V}$

$$I_B = \frac{10 - 0.7}{470000} = 19.8\text{ }\mu\text{A} \quad (1)$$

$$I_C = \beta I_B = \beta 19.8\text{ }\mu\text{A} \quad (2)$$

$$V_{CE} = 10 - 1500\beta I_B = 10 - 1500\beta (19.8 \times 10^{-6})\text{ V} \quad (3)$$

Table 1: Quiescent point parameter of circuit 1 for transistor with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$I_B$	19.8 $\mu\text{A}$	19.8 $\mu\text{A}$	0%
$I_C$	1.98 mA	2.46 mA	24%
$V_{CE}$	7.03 V	6.32 V	-10%

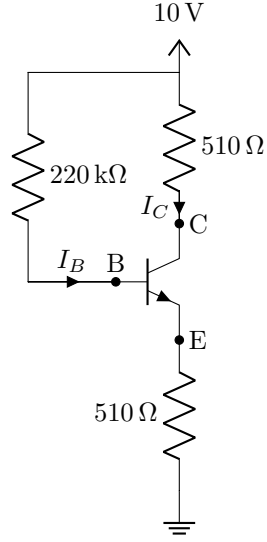


Figure 2: Circuit 2

Assuming  $V_{BE} = 0.7 \text{ V}$

$$I_E = (1 + \beta)I_B \quad (4)$$

$$10 \text{ V} = 220000I_B + 0.7 + 510(1 + \beta)I_B \quad (5)$$

$$I_B = \frac{9.3}{220510 + 510\beta} \quad (6)$$

$$I_C = \beta I_B = \frac{9.3\beta}{220510 + 510\beta} \quad (7)$$

$$V_{CE} = \left(10 - \frac{(510)(9.3)\beta}{220510 + 510\beta}\right) - \frac{510(1 + \beta)9.3}{220510 + 510\beta} \quad (8)$$

Table 2: Quiescent point parameters of circuit 2 for transistors with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$I_B$	34.3 $\mu\text{A}$	32.8 $\mu\text{A}$	-4%
$I_C$	3.43 mA	4.06 mA	18%
$V_{CE}$	6.49 V	5.84 V	-10%

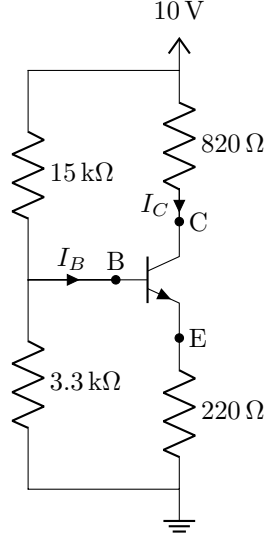


Figure 3: Circuit 3

Assuming  $V_{BE} = 0.7\text{ V}$

$$I_B = \frac{10 - V_B}{15000} - \frac{V_B}{3300} = \frac{20190 - 18300V_E}{49500000} \quad (9)$$

$$I_E = (1 + \beta)I_B = \frac{(1 + \beta)(20190 - 18300V_E)}{49500000} = \frac{V_E}{220} \quad (10)$$

$$V_E = \frac{44418000(1 + \beta)}{53526000 + 4026000\beta} \quad (11)$$

$$I_B = \frac{20190 - 18300 \frac{44418000(1 + \beta)}{53526000 + 4026000\beta}}{49500000} \quad (12)$$

$$I_C = \beta I_B \quad (13)$$

$$V_{CE} = V_C - V_E = (10 - 820I_C) - V_E \quad (14)$$

Table 3: Quiescent point parameters of circuit 3 for transistors with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$I_B$	44.3 $\mu\text{A}$	36.5 $\mu\text{A}$	-17%
$I_C$	4.42 mA	4.53 mA	2%
$V_{CE}$	5.39 V	5.28 V	-2%

## Result

### Circuit 1

The following is the experimental data obtained from circuit 1.

Table 4:  $V_B$ ,  $V_C$  and  $V_E$  of circuit 1 for transistor with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$V_B$	0.642 V	0.644 V	0%
$V_C$	5.984 V	5.552 V	-7%
$V_E$	0 V	0 V	0%

$I_B$ ,  $I_C$  and  $V_{BE}$  can be derived from the below equations,

$$I_B = \frac{10 - V_B}{470000} \quad (15)$$

$$I_C = \beta I_B \quad (16)$$

$$V_{CE} = V_C - V_E \quad (17)$$

Table 5: Quiescent point parameter of circuit 1 for transistor with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$I_B$	19.9 $\mu$ A	19.9 $\mu$ A	0%
$I_C$	1.99 mA	2.47 mA	24%
$V_{CE}$	5.984 V	5.552 V	-7%

## Circuit 2

The following is the experimental data obtained from circuit 2.

Table 6:  $V_B$ ,  $V_C$  and  $V_E$  of circuit 1 for transistor with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$V_B$	2.91 V	3.086 V	0%
$V_C$	7.74 V	7.56 V	-7%
$V_E$	2.296 V	2.467 V	0%

$I_B$ ,  $I_C$  and  $V_{BE}$  can be derived from the below equations,

$$I_B = \frac{10 - V_B}{220000} \quad (18)$$

$$I_C = \beta I_B \quad (19)$$

$$V_{CE} = V_C - V_E \quad (20)$$

Table 7: Quiescent point parameter of circuit 2 for transistor with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$I_B$	32.2 $\mu$ A	31.4 $\mu$ A	0%
$I_C$	3.22 mA	3.89 mA	20%
$V_{CE}$	5.444 V	5.093 V	-6%

### Circuit 3

The following is the experimental data obtained from circuit 3.

Table 8:  $V_B$ ,  $V_C$  and  $V_E$  of circuit 3 for transistor with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$V_B$	1.731 V	1.738 V	0%
$V_C$	6.031 V	6.008 V	0%
$V_E$	1.08 V	1.083 V	0%

$I_B$ ,  $I_C$  and  $V_{BE}$  can be derived from the below equations,

$$I_B = \frac{I_C}{\beta} \quad (21)$$

$$I_C = \frac{10 - V_C}{820} \quad (22)$$

$$V_{CE} = V_C - V_E \quad (23)$$

Table 9: Quiescent point parameter of circuit 3 for transistor with different  $\beta$

	$Q_1$	$Q_2$	% difference
$\beta$	100	124	24%
$I_B$	48.4 $\mu$ A	39.3 $\mu$ A	-18%
$I_C$	4.84 mA	4.87 mA	1%
$V_{CE}$	4.951 V	4.925 V	-1%

## Circuit 4



Figure 4: Oscilloscope output for circuit 4

$$\text{Gain} = \frac{1.61\text{V}}{18.1\text{mV}} = 89$$

## Conclusion

As demonstrated in this document above, circuit 3 setup is considerably stable across transistors with different  $\beta$  value compare to circuit 1 and circuit 2