

```
1 ECE2101L Lab7 Part B2: Measuring OUTPUT impedance of a black box with A to B open
2 * Author: Choi Tim Antony Yung
3 * Simulation with A to B open
4
5 .INCLUDE blackbox.cir
6
7 XBOX vth 0 BOX
8 .AC LIN 1 60 60
9 .PRINT AC v(vth)
10
11 .END
```