

ECE 4300  
Discrete System Design Using VHDL

Midterm 1

Choi Tim Antony Yung (ID:013499993)

March 10, 2021

# 1 Combinational Circuit

## Code

### D Flip-flop

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY DFlipflop IS
    PORT (
        D : IN STD_LOGIC;
        clk : IN STD_LOGIC;
        rst : IN STD_LOGIC;
        Q : OUT STD_LOGIC
    );
END DFlipflop;

ARCHITECTURE Behavioral OF DFlipflop IS
BEGIN

    PROCESS (clk, rst)
    BEGIN
        IF (rst = '1') THEN
            Q <= '0';
        ELSIF (rising_edge(clk)) THEN
            Q <= D;
        END IF;
    END PROCESS;

END Behavioral;
```

### Combinational Circuit

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY ECE4304_Midterm1_1 IS
    PORT (
        top_clk : IN STD_LOGIC;
        top_rst : IN STD_LOGIC;
        A : IN STD_LOGIC;
        B : IN STD_LOGIC;
        C : IN STD_LOGIC;
        D : IN STD_LOGIC;
        Z : OUT STD_LOGIC
    );
END ECE4304_Midterm1_1;

ARCHITECTURE Structural OF ECE4304_Midterm1_1 IS

    COMPONENT DFlipflop IS
        PORT (
```

```

        D : IN STD_LOGIC;
        clk : IN STD_LOGIC;
        rst : IN STD_LOGIC;
        Q : OUT STD_LOGIC
    );
END COMPONENT;

SIGNAL E : STD_LOGIC;
SIGNAL E_Q : STD_LOGIC;
SIGNAL F : STD_LOGIC;
SIGNAL F_Q : STD_LOGIC;

BEGIN

    E <= (A AND B AND C) OR D;
    F <= A NAND (B NOR C);

    EFF : DFlipflop
    PORT MAP(
        D => E,
        clk => top_clk,
        rst => top_rst,
        Q => E_Q
    );

    FFF : DFlipflop
    PORT MAP(
        D => F,
        clk => top_clk,
        rst => top_rst,
        Q => F_Q
    );

    Z <= E_Q XOR (NOT F_Q);

END Structural;

```

#### Testbench

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.math_real.ALL;
USE IEEE.numeric_std.ALL;

ENTITY ECE4304_Midterm1_1_tb IS
    -- Port ( );
END ECE4304_Midterm1_1_tb;

ARCHITECTURE Behavioral OF ECE4304_Midterm1_1_tb IS

    CONSTANT clock_period : TIME := 10 ns;

```

```

SIGNAL top_clk_tb : STD_LOGIC;
SIGNAL top_rst_tb : STD_LOGIC;
SIGNAL Z_tb : STD_LOGIC;
SIGNAL ctrl_tb : STD_LOGIC;

```

```

SIGNAL in_tb : STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL mismatch_tb : STD_LOGIC;

```

```

COMPONENT ECE4304_Midterm1_1 IS

```

```

    PORT (
        top_clk : IN STD_LOGIC;
        top_rst : IN STD_LOGIC;
        A : IN STD_LOGIC;
        B : IN STD_LOGIC;
        C : IN STD_LOGIC;
        D : IN STD_LOGIC;
        Z : OUT STD_LOGIC

```

```

    );

```

```

END COMPONENT;

```

```

BEGIN

```

```

    UUT : ECE4304_Midterm1_1

```

```

    PORT MAP(
        top_clk => top_clk_tb,
        top_rst => top_rst_tb,
        A => in_tb(3),
        B => in_tb(2),
        C => in_tb(1),
        D => in_tb(0),
        Z => Z_tb
    );

```

```

    CLK_GEN : PROCESS

```

```

    BEGIN

```

```

        top_clk_tb <= '1';
        WAIT FOR 0.5 * clock_period;
        top_clk_tb <= '0';
        WAIT FOR 0.5 * clock_period;

```

```

    END PROCESS;

```

```

    INIT_RST : PROCESS

```

```

    BEGIN

```

```

        top_rst_tb <= '1';
        WAIT FOR 0.5 * clock_period;
        top_rst_tb <= '0';
        WAIT;

```

```

    END PROCESS;

```

```

    TEST_MAIN : PROCESS

```

```

    BEGIN

```

```

        FOR i IN 0 TO 2 ** 4 - 1 LOOP -- all possible combination of 4 input

```

```

            in_tb <= STD_LOGIC_VECTOR(to_unsigned(i, 4));

```

```

            ctrl_tb <= ((in_tb(3) AND in_tb(2) AND in_tb(1)) OR in_tb(0)) XOR (in_tb(3) AND

```

```

        mismatch_tb <= Z_tb XOR ctrl_tb; -- can be found using "Next Transition" button
    WAIT FOR clock_period;
END LOOP;
END PROCESS;

```

```


END Behavioral;

```

## Simulation Result

As can be seen in figure 1, all possible input combination was simulated and the circuit behave as expected with no mismatch found.

Figure 1: Simulation Waveform of the Circuit

 

## 2 2-bit Comparator

Truth Table

$A_1$	$A_0$	$B_1$	$B_0$	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

## Karnaugh Maps

		$B_1B_0$			
		00	01	11	10
$A_1A_0$	00				
	01	1			
	11	1	1		1
	10	1	1		

		$B_1B_0$			
		00	01	11	10
$A_1A_0$	00	1			
	01		1		
	11			1	
	10				1

$$(A > B) = \overline{A_1} \overline{B_1} + \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_0}$$

$$(A = B) = \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + \overline{A_1} \overline{A_0} B_1 \overline{B_0} + \overline{A_1} A_0 B_1 B_0$$

$$= (A_1 \oplus B_1)(A_0 \oplus B_0)$$

		$B_1B_0$			
		00	01	11	10
$A_1A_0$	00		1	1	1
	01			1	1
	11				
	10			1	

$$(A < B) = \overline{A_1} B_0 + \overline{A_1} \overline{A_0} B_0 + \overline{A_0} B_1 B_0$$

$$= \overline{(A > B)} + \overline{(A = B)}$$

## Code

### Comparator Circuit

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY ECE4304_Midterm1_2 IS
    PORT (
        A : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        B : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        AGB : OUT STD_LOGIC; -- A>B
        AEB : OUT STD_LOGIC; -- A=B
        ALB : OUT STD_LOGIC; -- A<B
    );
END ECE4304_Midterm1_2;

ARCHITECTURE Structural OF ECE4304_Midterm1_2 IS

    SIGNAL AGB_temp : STD_LOGIC;
    SIGNAL AEB_temp : STD_LOGIC;

BEGIN

    AGB_temp <= (A(1) AND (NOT B(1))) OR
        (A(0) AND (NOT B(1)) AND (NOT B(0))) OR
        (A(1) AND A(0) AND (NOT B(0)));
    AEB_temp <= (A(1) XNOR B(1)) AND (A(0) XNOR B(0));
    AGB <= AGB_temp;
    AEB <= AEB_temp;
    ALB <= AGB_temp NOR AEB_temp;

END Structural;
```

### Testbench

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.math_real.ALL;
USE IEEE.numeric_std.ALL;

ENTITY ECE4304_Midterm1_2_tb IS
    -- Port ( );
END ECE4304_Midterm1_2_tb;

ARCHITECTURE Behavioral OF ECE4304_Midterm1_2_tb IS

    CONSTANT clock_period : TIME := 10 ns;
    SIGNAL top_clk_tb : STD_LOGIC;
    SIGNAL top_rst_tb : STD_LOGIC;
    SIGNAL AGB_tb : STD_LOGIC;
```



```

SIGNAL AEB_tb : STD_LOGIC;
SIGNAL ALB_tb : STD_LOGIC;
SIGNAL AGB_ctrl_tb : STD_LOGIC;
SIGNAL AEB_ctrl_tb : STD_LOGIC;
SIGNAL ALB_ctrl_tb : STD_LOGIC;

```

```

SIGNAL in_tb : STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL mismatch_tb : STD_LOGIC;

```

```

COMPONENT ECE4304_Midterm1_2 IS

```

```

    PORT (
        A : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        B : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        AGB : OUT STD_LOGIC; -- A>B
        AEB : OUT STD_LOGIC; -- A=B
        ALB : OUT STD_LOGIC -- A<B
    );

```

```

END COMPONENT;

```

```

BEGIN

```

```

    UUT : ECE4304_Midterm1_2

```

```

    PORT MAP(
        A => in_tb(3 DOWNTO 2),
        B => in_tb(1 DOWNTO 0),
        AGB => AGB_tb,
        AEB => AEB_tb,
        ALB => ALB_tb
    );

```

```

    CLK_GEN : PROCESS

```

```

    BEGIN
        top_clk_tb <= '1';
        WAIT FOR 0.5 * clock_period;
        top_clk_tb <= '0';
        WAIT FOR 0.5 * clock_period;
    END PROCESS;

```

```

    INIT_RST : PROCESS

```

```

    BEGIN
        top_rst_tb <= '1';
        WAIT FOR 0.5 * clock_period;
        top_rst_tb <= '0';
        WAIT;
    END PROCESS;

```

```

    TEST_MAIN : PROCESS

```

```

        VARIABLE A_int : INTEGER;
        VARIABLE B_int : INTEGER;
    BEGIN
        FOR i IN 0 TO 2 ** 4 - 1 LOOP -- all possible combination of 4 input
            in_tb <= STD_LOGIC_VECTOR(to_unsigned(i, 4));
            A_int := i/4;
            B_int := i MOD 4;

```

```

IF (A_int > B_int) THEN
    AGB_ctrl_tb <= '1';
ELSE
    AGB_ctrl_tb <= '0';
END IF;
IF (A_int = B_int) THEN
    AEB_ctrl_tb <= '1';
ELSE
    AEB_ctrl_tb <= '0';
END IF;
IF (A_int < B_int) THEN
    ALB_ctrl_tb <= '1';
ELSE
    ALB_ctrl_tb <= '0';
END IF;
mismatch_tb <= (AGB_ctrl_tb XOR AGB_tb) OR
    (AEB_ctrl_tb XOR AEB_tb) OR
    (ALB_ctrl_tb XOR ALB_tb);
-- can be found using "Next Transition" button in sim
WAIT FOR clock_period;
END LOOP;
END PROCESS;


END Behavioral;

```

## Simulation Result

As can be seen in figure 2, all possible input combination was simulated and the circuit behave as expected with no mismatch found.

Figure 2: Simulation Waveform of the Circuit

 

## 3 Clock Divider

### Code

#### D Flip-flop

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY DFlipflop IS
    PORT (
        D : IN STD_LOGIC;
        clk : IN STD_LOGIC;

```

```

        rst : IN STD_LOGIC;
        Q : OUT STD_LOGIC
    );
END DFlipflop;

ARCHITECTURE Behavioral OF DFlipflop IS
BEGIN

    PROCESS (clk, rst)
    BEGIN
        IF (rst = '1') THEN
            Q <= '0';
        ELSIF (rising_edge(clk)) THEN
            Q <= D;
        END IF;
    END PROCESS;

END Behavioral;

```

Clock Divider Circuit

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY ECE4304_Midterm1_3 IS
    PORT (
        clk200MHZ : IN STD_LOGIC;
        top_rst : IN STD_LOGIC;
        clk1M563HZ : OUT STD_LOGIC
    );
END ECE4304_Midterm1_3;

ARCHITECTURE Structural OF ECE4304_Midterm1_3 IS

    -- upcounter as clock divider circuit
    -- each flip-flop divide clock by 2
    --  $2^n * 1.563 = 200$ 
    -- with n being the number of flip-flop needed
    --  $\log(200/1.563)/\log(2) = \log(128)/\log(2) = 7$ 
    -- 7 flip-flops needed

    COMPONENT DFlipflop IS
        PORT (
            D : IN STD_LOGIC;
            clk : IN STD_LOGIC;
            rst : IN STD_LOGIC;
            Q : OUT STD_LOGIC
        );
    END COMPONENT;

    CONSTANT N : INTEGER := 7;
    SIGNAL top_Q : STD_LOGIC_VECTOR(N - 1 DOWNTO 0);
    SIGNAL top_notQ : STD_LOGIC_VECTOR(N - 1 DOWNTO 0);

```

```
SIGNAL top_clk_FF : STD_LOGIC_VECTOR(N - 1 DOWNT0 0);
```

```
BEGIN
```

```
top_notQ <= NOT top_Q;  
top_clk_FF <= top_notQ(N - 2 DOWNT0 0) & clk200MHZ; -- carry when falling edge  
clk1M563HZ <= top_Q(N - 1);  
DFF_GEN : FOR i IN 0 TO N - 1 GENERATE  
  BEGIN  
    DFF : DFlipflop  
    PORT MAP(  
      D => top_notQ(i), -- toggle each clock  
      clk => top_clk_FF(i),  
      rst => top_rst,  
      Q => top_Q(i)  
    );  
  END GENERATE;  
END Structural;
```

Testbench

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
USE IEEE.STD_LOGIC_UNSIGNED.ALL;  
USE IEEE.STD_LOGIC_ARITH.ALL;  
USE IEEE.math_real.ALL;  
USE IEEE.numeric_std.ALL;  
  
ENTITY ECE4304_Midterm1_3_tb IS  
  -- Port ( );  
END ECE4304_Midterm1_3_tb;  
  
ARCHITECTURE Behavioral OF ECE4304_Midterm1_3_tb IS  
  
  CONSTANT clock_period : TIME := 5 ns; -- 1/200MHZ is 5 ns  
  SIGNAL top_clk_tb : STD_LOGIC;  
  SIGNAL top_rst_tb : STD_LOGIC;  
  SIGNAL top_clk_out_tb : STD_LOGIC;  
  
  COMPONENT ECE4304_Midterm1_3 IS  
    PORT (  
      clk200MHZ : IN STD_LOGIC;  
      top_rst : IN STD_LOGIC;  
      clk1M563HZ : OUT STD_LOGIC  
    );  
  END COMPONENT;  
  
BEGIN  
  
  UUT : ECE4304_Midterm1_3  
  PORT MAP(  
    clk200MHZ => top_clk_tb,
```

```

        top_rst => top_rst_tb,
        clk1M563HZ => top_clk_out_tb
    );

    CLK_GEN : PROCESS
    BEGIN
        top_clk_tb <= '1';
        WAIT FOR 0.5 * clock_period;
        top_clk_tb <= '0';
        WAIT FOR 0.5 * clock_period;
    END PROCESS;

    INIT_RST : PROCESS
    BEGIN
        top_rst_tb <= '1';
        WAIT FOR 0.5 * clock_period;
        top_rst_tb <= '0';
        WAIT;
    END PROCESS;


END Behavioral;

```

## Simulation Result

As can be seen in figure 3, the generated clock have a frequency of  $f = \frac{1}{640\text{ ns}} = 1.5625\text{ MHz} \approx 1.563\text{ MHz}$

Figure 3: Simulation Waveform of the Circuit

 


## 4 Majority

### Truth Table

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>E</i>	<i>maj</i>
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	1

# Karnaugh Maps

 

## function

$$\text{maj}(A, B, C, D, E) = CDE + BDE + BCD + BCE + ACE + ACD + ABE + ABD + ABC + ADE$$

## Code

### Majority Circuit

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY ECE4304_Midterm1_4 IS
    PORT (
        A : IN STD_LOGIC;
        B : IN STD_LOGIC;
        C : IN STD_LOGIC;
        D : IN STD_LOGIC;
        E : IN STD_LOGIC;
        maj : OUT STD_LOGIC
    );
END ECE4304_Midterm1_4;

ARCHITECTURE Structural OF ECE4304_Midterm1_4 IS

    -- 5 input majority circuit output 1 when
    -- there are >= 3 input on high
    -- we can implement this as sum of product of
    -- all possible 3 input combinations since
    -- if there is no majority none of the products
    -- will output high, whereas if there is a majority
    -- at least three of the inputs will be high and will
    -- trigger at least one of the products

BEGIN

    maj <= (A AND B AND C) OR
            (A AND B AND D) OR
            (A AND B AND E) OR
            (A AND C AND D) OR
            (A AND C AND E) OR
            (A AND D AND E) OR
            (B AND C AND D) OR
            (B AND C AND E) OR
            (B AND D AND E) OR
            (C AND D AND E);

END Structural;
```

### Testbench

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.math_real.ALL;
USE IEEE.numeric_std.ALL;
```



**ENTITY** ECE4304\_Midterm1\_4\_tb **IS**

-- Port ( );

**END** ECE4304\_Midterm1\_4\_tb;

**ARCHITECTURE** Behavioral **OF** ECE4304\_Midterm1\_4\_tb **IS**

CONSTANT clock\_period : TIME := 10 ns;

SIGNAL top\_clk\_tb : STD\_LOGIC;

SIGNAL top\_rst\_tb : STD\_LOGIC;

SIGNAL in\_tb : STD\_LOGIC\_VECTOR(4 DOWNT0 0);

signal maj\_tb : std\_logic;

signal maj\_ctrl\_tb : std\_logic;

SIGNAL mismatch\_tb : STD\_LOGIC;

COMPONENT ECE4304\_Midterm1\_4 **IS**

**PORT** (

A : **IN** STD\_LOGIC;

B : **IN** STD\_LOGIC;

C : **IN** STD\_LOGIC;

D : **IN** STD\_LOGIC;

E : **IN** STD\_LOGIC;

maj : **OUT** STD\_LOGIC

);

**END** COMPONENT;

**BEGIN**

UUT : ECE4304\_Midterm1\_4

**PORT** MAP(

A => in\_tb(4),

B => in\_tb(3),

C => in\_tb(2),

D => in\_tb(1),

E => in\_tb(0),

maj => maj\_tb

);

CLK\_GEN : PROCESS

**BEGIN**

top\_clk\_tb <= '1';

WAIT FOR 0.5 \* clock\_period;

top\_clk\_tb <= '0';

WAIT FOR 0.5 \* clock\_period;

**END** PROCESS;

INIT\_RST : PROCESS

**BEGIN**

top\_rst\_tb <= '1';

WAIT FOR 0.5 \* clock\_period;

top\_rst\_tb <= '0';

WAIT;

**END** PROCESS;

```

TEST_MAIN : PROCESS
    variable high_num: integer;
BEGIN
    FOR i IN 0 TO 2 ** 5 - 1 LOOP -- all possible combination of 4 input
        in_tb <= STD_LOGIC_VECTOR(to_unsigned(i, 5));
        high_num := i/2**4 + ((i/2**3) mod 2)+ ((i/2**2) mod 2)+ ((i/2**1) mod 2)+ (i mod 2);
        if (high_num > 2) then maj_ctrl_tb <= '1'; else maj_ctrl_tb <= '0'; end if;
        mismatch_tb <= maj_tb xor maj_ctrl_tb;
        -- can be found using "Next Transition" button in sim
        WAIT FOR clock_period;
    END LOOP;
END PROCESS;


END Behavioral;

```

## Simulation Result

As can be seen in figure 4, all possible input combination was simulated and the circuit behave as expected with no mismatch found.

Figure 4: Simulation Waveform of the Circuit

 


## 5 N-bit Generic Multiplier

### 5.a Theory

Full Adder can be used to compose a multiplier as seen in 5

Figure 5: Sketch

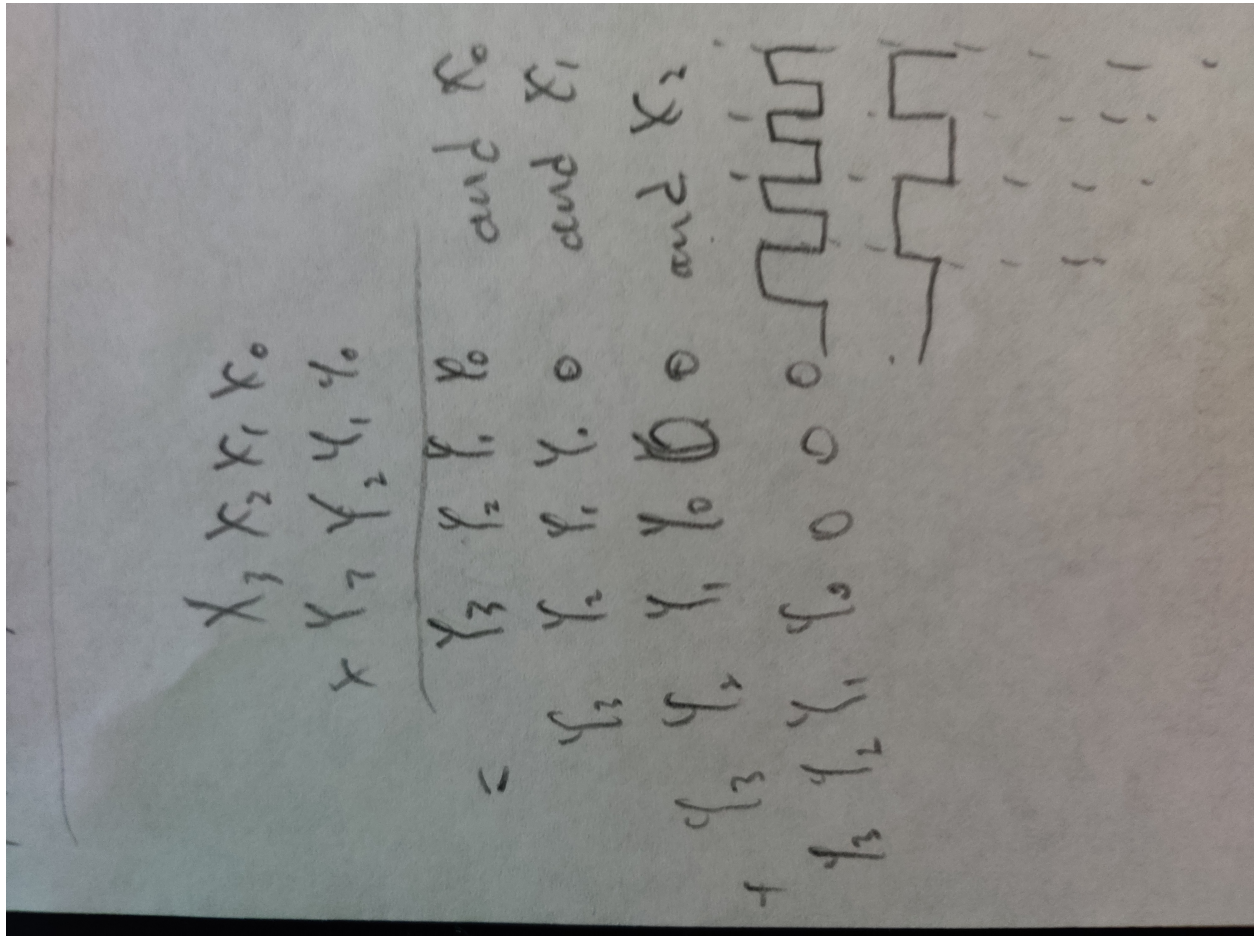

### Code

N-bit Full Adder

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NFA IS
    GENERIC (N : INTEGER := 1);
    PORT (
        cin : IN STD_LOGIC;
        X : IN STD_LOGIC_VECTOR(N - 1 DOWNTO 0);
        Y : IN STD_LOGIC_VECTOR(N - 1 DOWNTO 0);
        S : OUT STD_LOGIC_VECTOR(N - 1 DOWNTO 0);
        cout : OUT STD_LOGIC
    );
END NFA;
```

```

    );
END NFA;

ARCHITECTURE Structural OF NFA IS

    SIGNAL C : STD_LOGIC_VECTOR(N DOWNT0 0);

BEGIN

    cout <= C(N);
    C(0) <= cin;
    FA_GEN : FOR i IN 0 TO N - 1 GENERATE
        C(i + 1) <= (X(i) AND Y(i)) OR (X(i) AND C(i)) OR (Y(i) AND C(i));
        S(i) <= X(i) XOR Y(i) XOR C(i);
    END GENERATE;

END Structural;

```

### Majority Circuit

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY ECE4304_Midterm1_5 IS
    GENERIC (N : INTEGER := 3);
    PORT (
        X : IN STD_LOGIC_VECTOR(N - 1 DOWNT0 0);
        Y : IN STD_LOGIC_VECTOR(N - 1 DOWNT0 0);
        P : OUT STD_LOGIC_VECTOR((2 * N) - 1 DOWNT0 0)
    );
END ECE4304_Midterm1_5;

ARCHITECTURE Structural OF ECE4304_Midterm1_5 IS

    COMPONENT NFA IS
        GENERIC (N : INTEGER := N);
        PORT (
            cin : IN STD_LOGIC;
            X : IN STD_LOGIC_VECTOR(N - 1 DOWNT0 0);
            Y : IN STD_LOGIC_VECTOR(N - 1 DOWNT0 0);
            S : OUT STD_LOGIC_VECTOR(N - 1 DOWNT0 0);
            cout : OUT STD_LOGIC
        );
    END COMPONENT;

    TYPE vector_array IS ARRAY (N - 1 DOWNT0 0) OF STD_LOGIC_VECTOR((2 * N) - 1 DOWNT0 0);
    SIGNAL sum_vecar : vector_array;
    SIGNAL X_expand_vecar : vector_array; -- expand X(i) to match width for bitwise and
    SIGNAL summand_vecar : vector_array;

BEGIN

    P <= sum_vecar(N - 1);

```

```

X_expand_vecar(0) <= (OTHERS => X(0)); -- expand X(i) to match width for bitwise and
SIG_PREP_1 : FOR i IN 0 TO N - 1 GENERATE
BEGIN
    sum_vecar(0)(i) <= Y(i) AND X_expand_vecar(0)(i);
END GENERATE;
sum_vecar(0)(N) <= '0';

SIG_PREP : FOR i IN 1 TO N - 1 GENERATE
BEGIN
    X_expand_vecar(i) <= (OTHERS => X(i)); -- expand X(i) to match width for bitwise and
    summand_vecar(i)(N + i - 1 DOWNT0 i) <= X_expand_vecar(i)(N + i - 1 DOWNT0 i) AND Y(i);
    summand_vecar(i)(i - 1 DOWNT0 0) <= (OTHERS => '0');
    summand_vecar(i)(N + i) <= '0';
END GENERATE;

NFA_GEN : FOR i IN 1 TO N - 1 GENERATE
BEGIN
    NFAUnit : NFA
    GENERIC MAP(N => N + i)
    PORT MAP(
        cin => '0',
        X => sum_vecar(i - 1)(N - 1 + i DOWNT0 0),
        Y => summand_vecar(i)(N - 1 + i DOWNT0 0),
        S => sum_vecar(i)(N - 1 + i DOWNT0 0),
        cout => sum_vecar(i)(N + i)
    );
END GENERATE;
END Structural;

```

## Testbench

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.math_real.ALL;
USE IEEE.numeric_std.ALL;

ENTITY ECE4304_Midterm1_5_tb IS
    -- Port ( );
END ECE4304_Midterm1_5_tb;

ARCHITECTURE Behavioral OF ECE4304_Midterm1_5_tb IS

    CONSTANT clock_period : TIME := 10 ns;
    CONSTANT N_tb : INTEGER := 3;

    SIGNAL top_clk_tb : STD_LOGIC;
    SIGNAL top_rst_tb : STD_LOGIC;

    SIGNAL X_tb : STD_LOGIC_VECTOR(N_tb - 1 DOWNT0 0);
    SIGNAL Y_tb : STD_LOGIC_VECTOR(N_tb - 1 DOWNT0 0);

```

```
SIGNAL P_tb : STD_LOGIC_VECTOR((2 * N_tb) - 1 DOWNTO 0);
```

```
SIGNAL mismatch_tb : STD_LOGIC;
```

```
COMPONENT ECE4304_Midterm1_5 IS
```

```
  GENERIC (N : INTEGER := N_tb);
```

```
  PORT (
```

```
    X : IN STD_LOGIC_VECTOR(N - 1 DOWNTO 0);
```

```
    Y : IN STD_LOGIC_VECTOR(N - 1 DOWNTO 0);
```

```
    P : OUT STD_LOGIC_VECTOR((2 * N) - 1 DOWNTO 0)
```

```
  );
```

```
END COMPONENT;
```

```
BEGIN
```

```
  UUT : ECE4304_Midterm1_5
```

```
  GENERIC MAP(N => N_tb)
```

```
  PORT MAP(
```

```
    X => X_tb,
```

```
    Y => Y_tb,
```

```
    P => P_tb
```

```
  );
```

```
  CLK_GEN : PROCESS
```

```
  BEGIN
```

```
    top_clk_tb <= '0';
```

```
    WAIT FOR 0.5 * clock_period;
```

```
    top_clk_tb <= '1';
```

```
    WAIT FOR 0.5 * clock_period;
```

```
  END PROCESS;
```

```
  INIT_RST : PROCESS
```

```
  BEGIN
```

```
    top_rst_tb <= '1';
```

```
    WAIT FOR 0.5 * clock_period;
```

```
    top_rst_tb <= '0';
```

```
    WAIT;
```

```
  END PROCESS;
```

```
  TEST_MAIN : PROCESS
```

```
  BEGIN
```

```
    FOR i IN 0 TO 2 ** N_tb - 1 LOOP -- all possible combination of inputs
```

```
      FOR j IN 0 TO 2 ** N_tb - 1 LOOP
```

```
        X_tb <= STD_LOGIC_VECTOR(to_unsigned(i, N_tb));
```

```
        Y_tb <= STD_LOGIC_VECTOR(to_unsigned(j, N_tb));
```

```
        WAIT FOR clock_period;
```

```
        IF (conv_integer(P_tb) = i * j) THEN
```

```
          mismatch_tb <= '0';
```

```
        ELSE
```

```
          mismatch_tb <= '1';
```

```
        END IF;
```

```
      END LOOP;
```

```
    END LOOP;
```

```
  END PROCESS;
```

END Behavioral;

Simulation Result

As can be seen in figure 6 and 7, all possible input combination was simulated and the circuit behave as expected with no mismatch found.

Figure 6: Simulation Waveform of the Circuit

 


Figure 7: Simulation Waveform of the Circuit

