

ECE 2200L
Introduction to Microelectronics Circuits
Laboratory

Experiment 5
Bipolar Junction Transistor Current-Voltage
Characteristics

Report

Choi Tim Antony Yung

October 14, 2020

Objective

To study the current-voltage relationships of the bipolar junction transistors through laboratory experimentation.

Result

The following is the experimental data obtained from 1N2222 BJT.

Table 1: I_B and V_{BE} values at circuit without $500\ \Omega$ resistor at collector

V_{BE}	I_B
0 mV	0 μ A
639 mV	10 μ A
658 mV	20 μ A
668 mV	30 μ A
676 mV	40 μ A
682 mV	50 μ A
686 mV	60 μ A
689 mV	70 μ A
692 mV	80 μ A
695 mV	90 μ A
698 mV	100 μ A

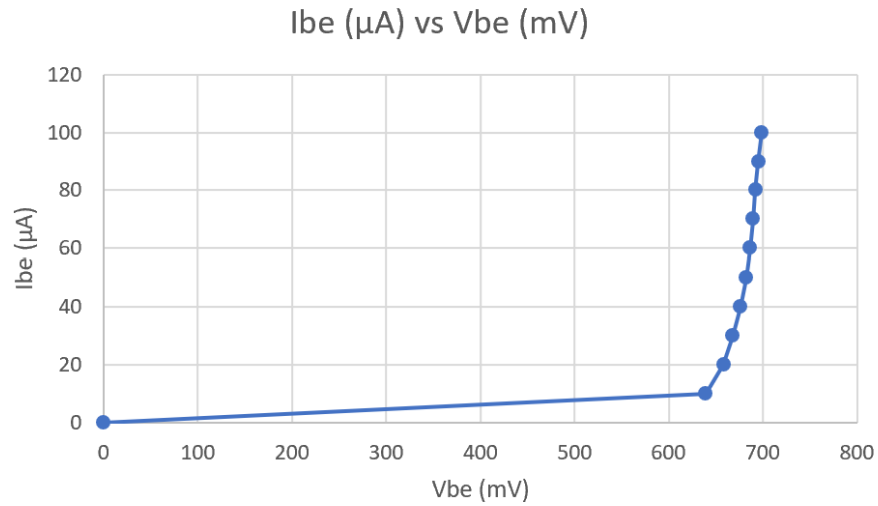


Figure 1: I_B vs V_{BE} chart of 1N2222 at circuit without $500\ \Omega$ resistor at collector

Table 2: I_C and V_{CE} values at circuit with 500Ω resistor at collector

V_{CE}	$I_B = 20\mu A$		$I_B = 40\mu A$		$I_B = 60\mu A$	
	V_{CC}	I_C	V_{CC}	I_C	V_{CC}	I_C
1 V	2.28 V	0.002 296 A	3.64 V	0.004 736 A	4.97 V	0.007 122 A
3 V	4.31 V	0.002 350 A	5.72 V	0.004 880 A	7.05 V	0.007 266 A
5 V	6.31 V	0.002 350 A	7.83 V	0.005 077 A	9.28 V	0.007 679 A
7 V	8.36 V	0.002 440 A	9.93 V	0.005 257 A	11.43 V	0.007 948 A
9 V	10.37 V	0.002 458 A	11.99 V	0.005 364 A	13.67 V	0.008 378 A
11 V	12.4 V	0.002 512 A	13.98 V	0.005 346 A	15.95 V	0.008 881 A

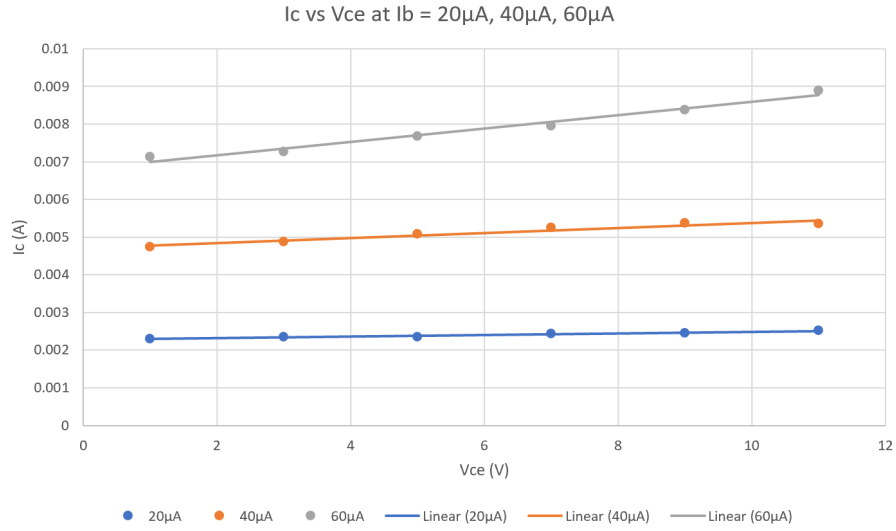


Figure 2: I_C vs V_{CE} chart of 1N2222 at circuit with 500Ω resistor at collector

DC β at operating point of $V_{CE} = 5\text{ V}$ and $I_B = 40\mu A$ can then be derived.

$$\beta_{DC} = \frac{I_C(V_{CE} = 5\text{ V}, I_B = 40\mu A)}{I_B = 40\mu A} = \frac{0.005\,077\text{ A}}{0.000\,040\text{ A}} = 126.925 \quad (1)$$

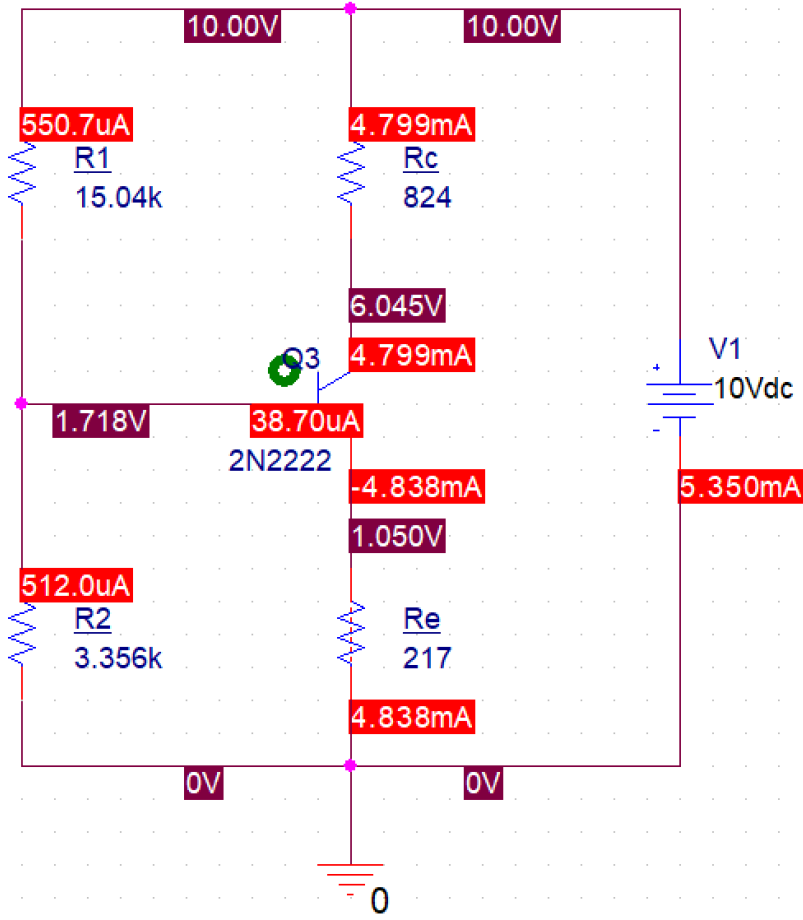


Figure 3: PSpice simulation with bias display of the circuit

R_1	=	15.04 k Ω
R_2	=	3.356 k Ω
R_E	=	217 k Ω
R_C	=	824 k Ω
V_{CC}	=	10.00 V
V_C	=	5.98 V
V_E	=	1.067 V
V_B	=	1.719 V

Table 3: Values from circuit

R_1	=	15.04 k Ω
R_2	=	3.356 k Ω
R_E	=	217 k Ω
R_C	=	824 k Ω
V_{CC}	=	10.00 V
V_C	=	6.045 V
V_E	=	1.050 V
V_B	=	1.718 V

Table 4: Values from simulation

Assuming I_B , I_C enter and I_E exit the BJT, for this circuit,

$$I_C = \frac{V_{CC} - V_C}{R_C}$$

$$I_B = I_E - I_C = \frac{V_E}{R_E} - \frac{V_{CC} - V_C}{R_C}$$

$$V_{CE} = V_C - V_E$$

$$\beta = \frac{I_C}{I_B}$$

We can then calculate β and the BJT bias point I_B , I_C and V_{CE} from table 3 and table 4.

I_C	=	4.88 mA
I_B	=	38.4 μ A
V_{CE}	=	4.913 V
β	=	127.1

Table 5: Derived from circuit

I_C	=	4.799 mA
I_B	=	38.70 μ A
V_{CE}	=	4.995 V
β	=	124

Table 6: Derived from simulation

Conclusion

From equation 1 we found that $\beta = 126.925$, which is close to the value from table 5. The experimental value at table 3 and table 5 are also similar to the values obtain from PSpice simulation listed in table 4 and table 6.