

ECE 2101L
Electrical Circuit Analysis II Laboratory


Lab 12
Maximum Power Transfer and Power Factor
Correction

Prelab

Choi Tim Antony Yung

April 27, 2020

1 Maximum power transfer

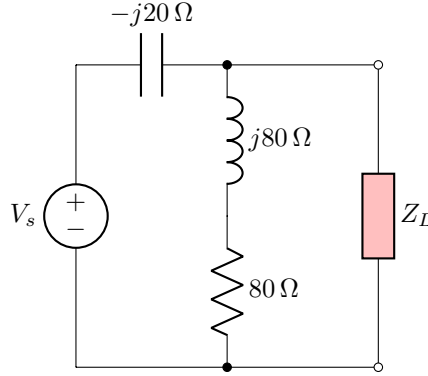

Z_L required to maximize power transfer is the complex conjugate of the Thevenin impedance between the two terminal of the load impedance.

$$Z_L = \left(\frac{1}{\frac{1}{80+j80} + \frac{1}{-j20}} \right)^* = 3.2 + j22.4 \Omega$$

$$S_{max} = \frac{|V_L|^2}{Z_L^*} = \frac{\left| \frac{\frac{200\sqrt{2}}{\sqrt{2}} \frac{1}{\frac{1}{80+j80} + \frac{1}{3.2+j22.4}}}{\frac{1}{80+j80} + \frac{1}{3.2+j22.4} - j20} \right|^2}{3.2 - j22.4} = \frac{640000}{3.2 - j22.4} = 4000 + j28000 \text{ VA}$$

$$P_{max} = 4000 \text{ W}$$

2 Power factor correction

Given $I = 10/\underline{9.2^\circ}$ and $V = 240/\underline{62^\circ}$

$$S = \frac{1}{2} V_m I_m / \underline{\theta_v - \theta_i} = \frac{1}{2} (240)(10) / \underline{62^\circ - 9.2^\circ}$$

$$S = 1200 / \underline{52.8^\circ} = 725.5 + j955.8 \text{ VA}$$

Apparent Power

$$|S| = 1200 \text{ VA}$$

Real Power

$$P = 725.5 \text{ W}$$

Reactive Power

$$Q = 955.8 \text{ VAR}$$

Power Factor

$$PF = \cos(\theta_v - \theta_i) = \cos(52.8^\circ) = 0.6046$$

The capacitance required to 0.97 lagging can be determined as follow,

$$C = \frac{1}{\omega|Z_C|} = \frac{Q_c}{\omega V_{rms}^2} = \frac{Q - P \tan(\cos^{-1}(0.97))}{\omega V_{rms}^2}$$

$$C = \frac{955.8 - (725.5)(0.2506)}{28800\omega} = \frac{0.02687}{\omega} \text{ F}$$