

ECE 2200L
Introduction to Microelectronics Circuits
Laboratory

Experiment 8
MOSFET Biasing Stability and Signaling

Report

Choi Tim Antony Yung

November 4, 2020

Objective

To design a 4-resistor biasing circuit to meet specification with a pre existing MOSFET from the earlier Lab (Lab7).

Prelab

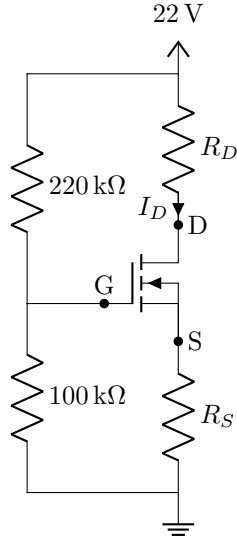


Figure 1: Circuit of Step 1 and Step 2

Given $V_T = 1.6 \text{ V}$ and $K_n = 0.1 \text{ mA/V}^2$, we can determine the value of R_D and R_S such that the circuit is biased to a Q-point of $I_{Dq} = 2.5 \text{ mA}$ and $V_{DSq} = 8 \text{ V}$

$$V_G = (22 \text{ V}) \frac{100000}{220000 + 100000} = 6.875 \text{ V} \quad (1)$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_T)^2 \quad (2)$$

$$2.5 = \frac{0.1}{2} (V_{GS} - 1.6)^2 \quad (3)$$

$$V_{GS} = 1.758 \text{ V} \quad (4)$$

$$V_S = V_G - V_{GS} = 5.117 \text{ V} \quad (5)$$

$$R_S = \frac{5.117 \text{ V}}{2.5 \text{ mA}} = 2.05 \text{ k}\Omega \approx 2.2 \text{ k}\Omega \quad (6)$$

$$R_D = \frac{22 - V_D}{I_D} = \frac{(22 - (8 + 5.117)) \text{ V}}{2.5 \text{ mA}} = \frac{8.885 \text{ V}}{2.5 \text{ mA}} = 3.553 \text{ k}\Omega \approx 3.9 \text{ k}\Omega \quad (7)$$

Procedure

Step 1

Circuit in figure 1 was constructed with MOSFET with $V_T = 1.6 \text{ V}$ and $K_n = 0.1 \text{ mA/V}^2$. V_D , V_G and V_S was measured in order to determine Q-point parameter I_{Dq} and V_{DSq} .

$$V_D = 13.00 \text{ V}$$

$$V_G = 6.8 \text{ V}$$

$$V_S = 5.01 \text{ V}$$

From the above values I_{Dq} and V_{DSq} can be found

$$V_{DSq} = 13.00 - 5.01 = 7.99 \text{ V, a } -0.125\% \text{ difference from specification}$$

$$I_{Dq} = \frac{22 - 13.00}{3900} = 2.3 \text{ mA, a } -8\% \text{ difference from specification}$$

Step 2

Circuit 1 was then constructed with a different MOSFET. V_D , V_G and V_S was measured in order to determine Q-point parameter I_{Dq} and V_{DSq} .

$$V_D = 12.67 \text{ V}$$

$$V_G = 6.8 \text{ V}$$

$$V_S = 5.2 \text{ V}$$

From the above values I_{Dq} and V_{DSq} can be found

$$V_{DSq} = 12.67 - 5.2 = 7.47 \text{ V, a } -6.51\% \text{ difference from}$$

$$I_{Dq} = \frac{22 - 12.67}{3900} = 2.39 \text{ mA, a } 3.91\% \text{ difference from specification}$$

Step 3

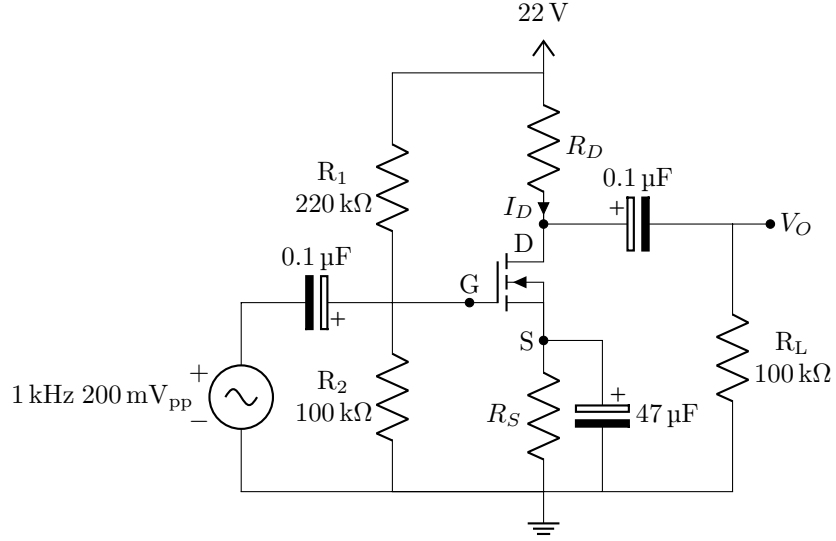


Figure 2: Circuit of Step 3

Given $V_T = 1.6 \text{ V}$ and $K_n = 0.1 \text{ mA/V}^2$ and a Q-point at $I_{Dq} = 2.5 \text{ mA}$ and $V_{DSq} = 8 \text{ V}$, we can calculate the small signal transconductance g_m as follow

$$I_D = \frac{K_n}{2} (V_{GS} - V_T)^2$$

$$\sqrt{\frac{2}{K_n} I_D} = (V_{GS} - V_T)$$

$$g_m = \frac{\delta I_D}{\delta V_{GS}} = K_n (V_{GS} - V_T) = \sqrt{2 K_n I_{Dq}} = 22.36 \text{ mS}$$

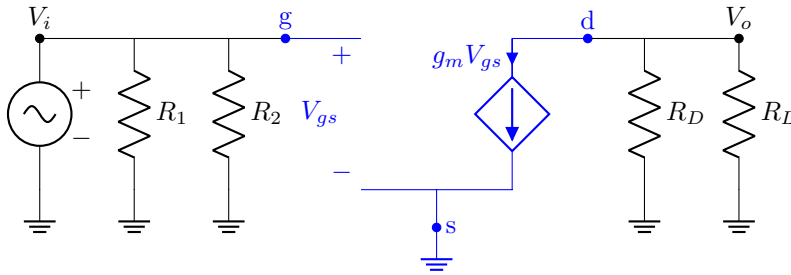


Figure 3: Circuit in Step 3 using small signal model MOSFET (blue)

Using the small signal model, $A_V = \frac{V_o}{V_i}$ can then be derived

$$\begin{aligned}
 V_i &= V_{gs} \\
 V_o &= -g_m V_{gs} (R_D || R_L) \\
 A_V &= \frac{V_o}{V_i} = -g_m (R_D || R_L) \\
 A_V &= -(22.36 \text{ mS})(3.9 \text{ k}\Omega || 100 \text{ k}\Omega) = -83.93
 \end{aligned}$$

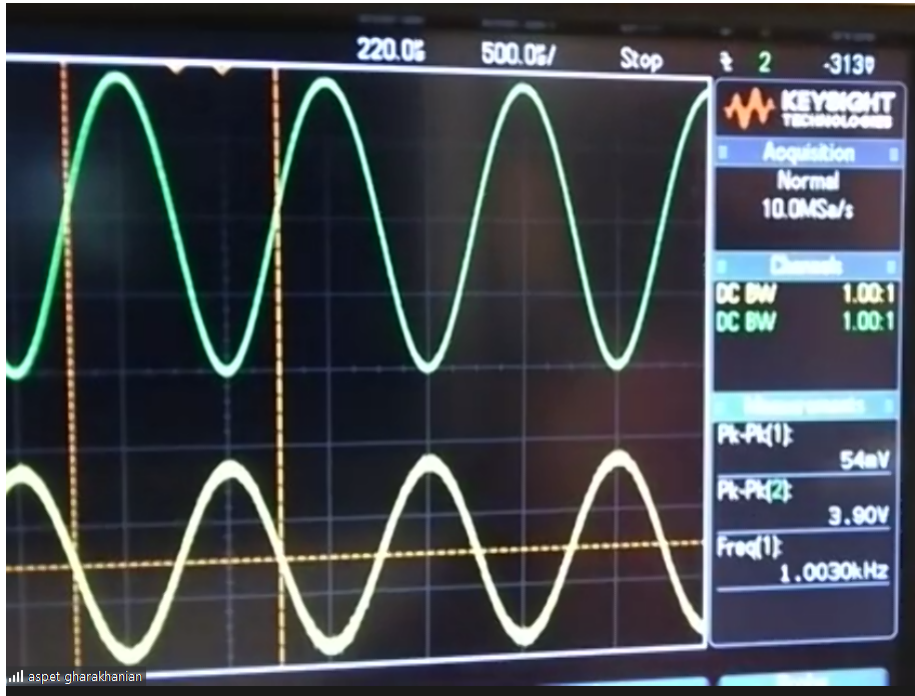


Figure 4: Oscilloscope output of Step 3 circuit (Figure 2) showing $V_{i_{pp}} = 54 \text{ mV}$ and $V_{o_{pp}} = 3.90 \text{ V}$

From the Oscilloscope the experimental value of A_V can be calculated

$$A_V = -\frac{3900}{54} \approx -72.22, \text{ a } -14.0\% \text{ difference from theoretical value}$$

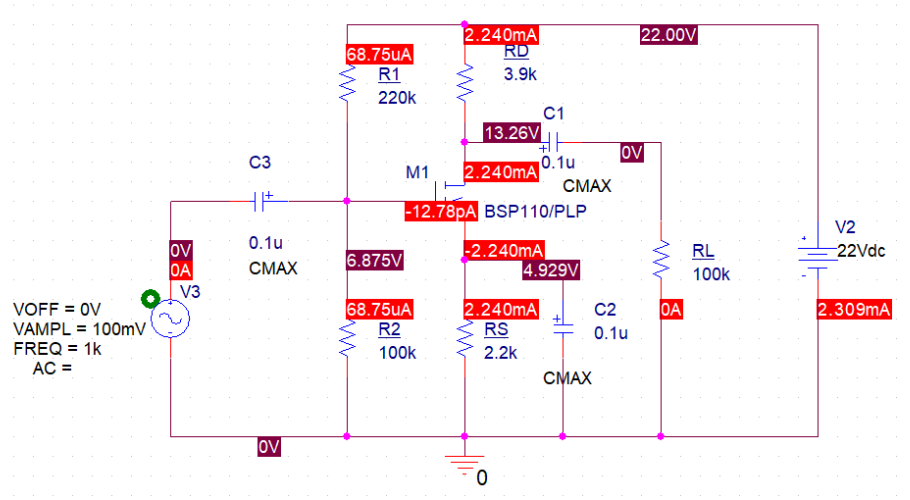


Figure 5: PSpice simulation of Step 3 circuit

Conclusion

As demonstrated above, change in K_n and V_T in a bias circuit designed for a specific MOSFET affects the resulting Q-point parameters.