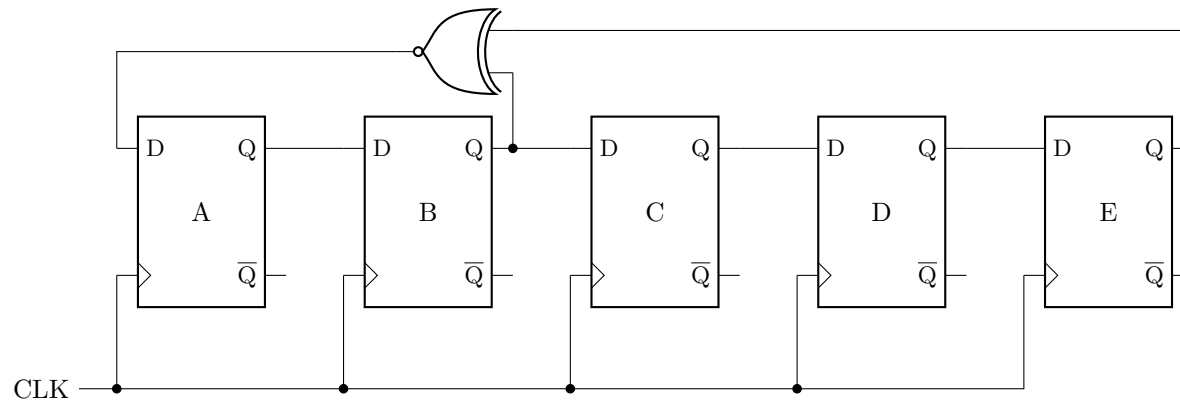# ECE 2300
# Digital Logic Design

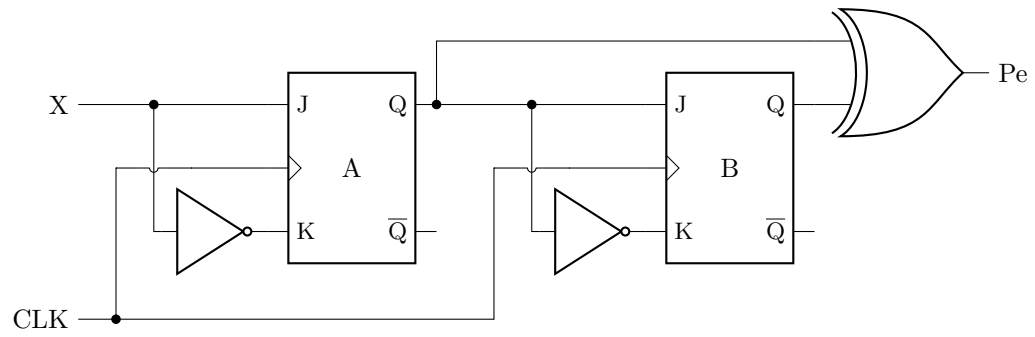## Homework 8

Choi Tim Antony Yung

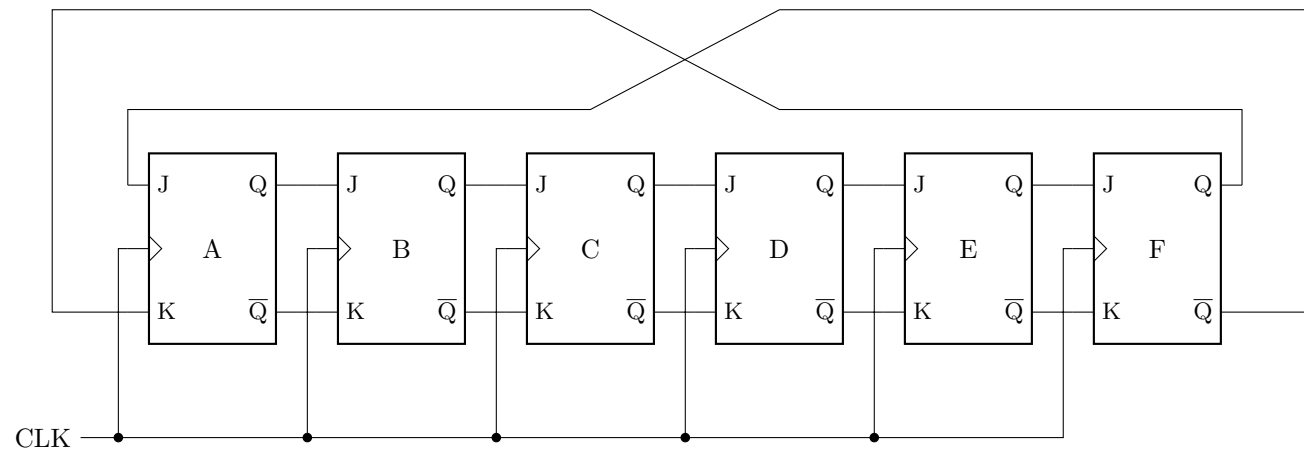April 27, 2020
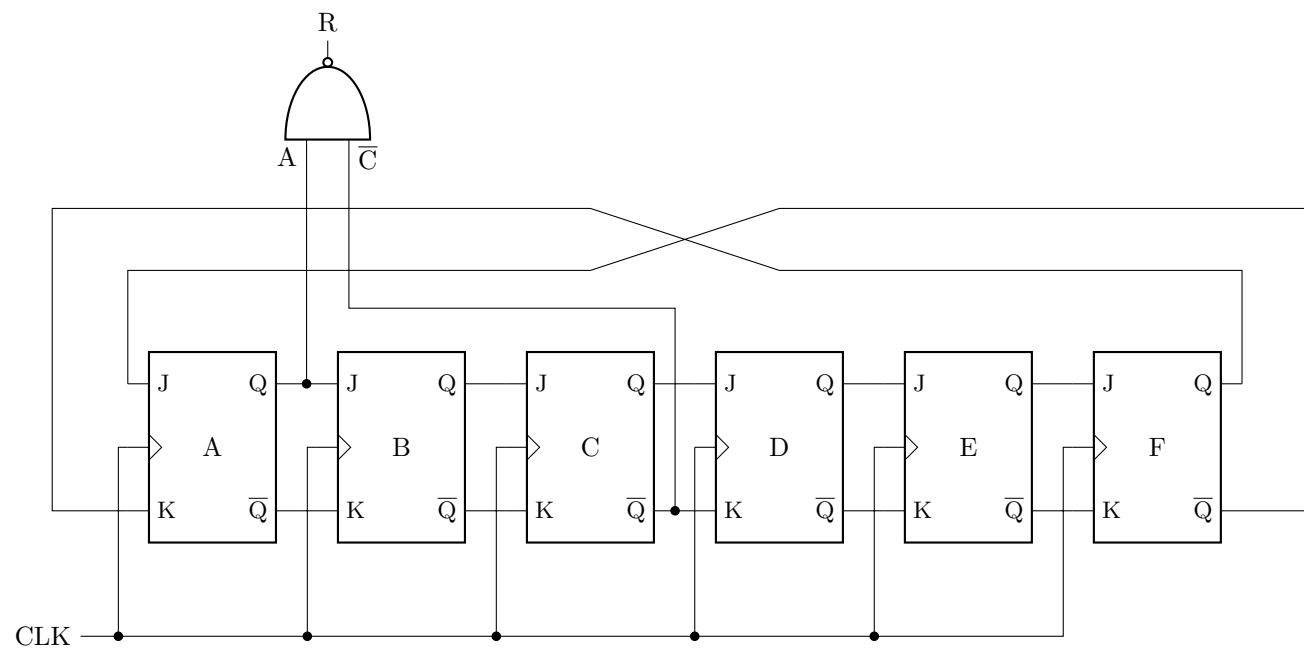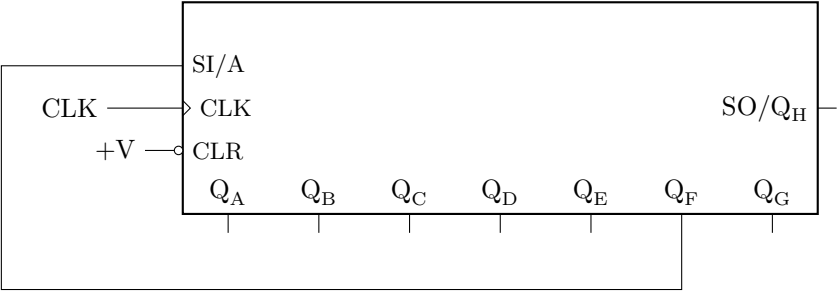
**2a**

**3a**

**5a**

**5c**

**6a**

**6a**